

# A TVT For Your KIM

... at a price you won't believe

**H**ere is the great happening in TVT technology you have long been waiting for. Take a small, single-sided PC card with SIX integrated circuits on it, plug it into your KIM-1 or other microcomputer and display up to several thousand upper and lower case characters of your choice, all on an ordinary TV set with minimum modifications. Despite its "all the bells and whistles" performance, the cost of this new TVT approach is so ludicrously low that there's no comparing it with anything previously available. *If you're a real dyed-in-the-wool scrounger* (etch your own boards, steal sockets and connectors, burn your own PROMs, etc. . . .), you can put this together for around nine dollars plus the rapidly dropping cost of a character generator IC!

Complete kits and ready-to-go units are also available commercially, at somewhat higher but still unbelievable prices.

This new TVT development uses the microcomputer to do practically *all* of the

system timing and control involved in a video display. This reduces the remaining interface circuitry to three hex inverters, two baby PROMs, and a character generator. Your computer alternates its compute and display modes, just as your KIM-1 now alternates between computer and keyboard modes. With fancy enough software, you can make this alteration nearly or completely transparent. More simply, you let the screen go blank when the computer is busy and doesn't want to talk to you anyway.

An entire book could be written on this whole new TVT ballgame. In fact . . . the book is called *Microprocessor Based Video Displays*, and Sams will print it. What we'll do here is lift just enough out of the book to show you how to build a video display for your KIM-1. The particular circuit is called a TVT-6L (L for lower case) and we'll show you how to build displays of 16 lines of 32 characters, 13 lines of 64 characters, and 25 lines of 64

characters, along with a fancy full-performance cursor that includes scrolling, erase to end of screen, full motions, and the usual goodies. The larger displays will take more memory than the bare bones KIM-1 has, so we'll show you one way to go with a KIM-1 and KIM-2 (4K add-on RAM) pair of cards.

## How It Works

The block diagram of the TVT-6L is shown in Fig. 1a. An area of your microcomputer's regular memory is reserved for your display. On the minimum KIM-1, a 512 character, 16 x 32 display on pages 02 and 03 is a good starting point, although the TVT-6L card can work with any contiguous memory block from 0000 to 0FFF. Since the KIM uses parts of page 00 and 01 for its operating system, these usually aren't available for alphanumeric display use. For the larger displays with added RAM, memory locations from pages four through seven or else four through ten (0400-07FF or 0400-0AFF)

are a good choice.

Besides these display memory pages, you'll need a place to put the SCAN program that tricks the KIM-1 and a TV set into talking to each other compatibly. Usually your SCAN program is around ninety words long. On the KIM-1, this is easily stuffed into the leftover scratchpad RAM starting at 1780.

Our DECODE read only memory is the heart of our TVT circuit. This PROM is activated by sending it an address from 2000 to EFFF. When activated, the DECODE memory causes a companion SCAN memory to force the microcomputer into a *scan* mode that advances the CPU's program counter 32, 64, or some other number of selected steps, *advancing once each microsecond*, binary counter style.

During this active horizontal scan time of usually 32 or 64 microseconds, all the memory in the microcomputer is sequentially interrogated on a *one memory slot per microsecond* basis. A new *upstream tap* is added to the memory to be displayed that *always* outputs data to the TVT-6L circuit, even and particularly when the display memory does NOT have access to the data bus.

So, during a scan mode, the display memory outputs characters to the TVT even though it does not have control of the data bus. The characters have the format shown in Fig. 1b, with an ASCII character using up the lower seven bits of the memory word. An optional cursor bit is placed on bit eight if wanted or needed. A zero in bit eight does nothing; a one optionally displays a winking cursor under both software and hardware control.

The lower seven bits of a character that were sent from the upstream tap go to a character generator IC1. IC1 also receives some "what row of dots do we want?" information from the DECODE

read only memory IC2. This particular character generator has an internal video shift register to directly output serial video in a 7 x 11 dot matrix with descenders format. The internal video shift register in IC1 derives its load and clock timing pulses from the KIM system clock  $\phi 2$  by way of gated oscillator IC6.

The serial output video goes now to a new, simple, and super-important circuit called a *bandwidth enhancer* in IC5. The bandwidth enhancer *predistorts* the output video to exactly cancel the way your TV set is going to try and mess it up. With this circuit, it's a simple matter to output several thousand characters per frame and still stay within the ordinary video bandwidth of a plain old TV set. Our bandwidth enhancer simply makes the dots longer than the undots, with the amount of lengthening set by a CLARITY control that is tuned to your TV for the sharpest and brightest display.

Meanwhile, two other outputs from the DECODE memory IC2 go to a position delay circuit in IC4 to provide horizontal and vertical positioning. The delayed sync signals are combined with the enhanced video in *video combiner* IC5.

IC5 gives us *two* outputs. One is the usual monitor output with grounded sync tips and +2 volt white level, used with monitors and completely preconverted TV sets. Our second TV output is translated upwards to put the white level at +4 volts, the usual bias level needed to go *directly* into the base of the first video amplifier transistor in a portable, transformer operated, solid state, black and white TV. Thus, our TV output greatly simplifies direct video interface. As Fig. 7 will show us later on, all you do is rip off the headphone jack and use it as an automatic video changeover switch, defeat the sound trap, and that's all you need — at

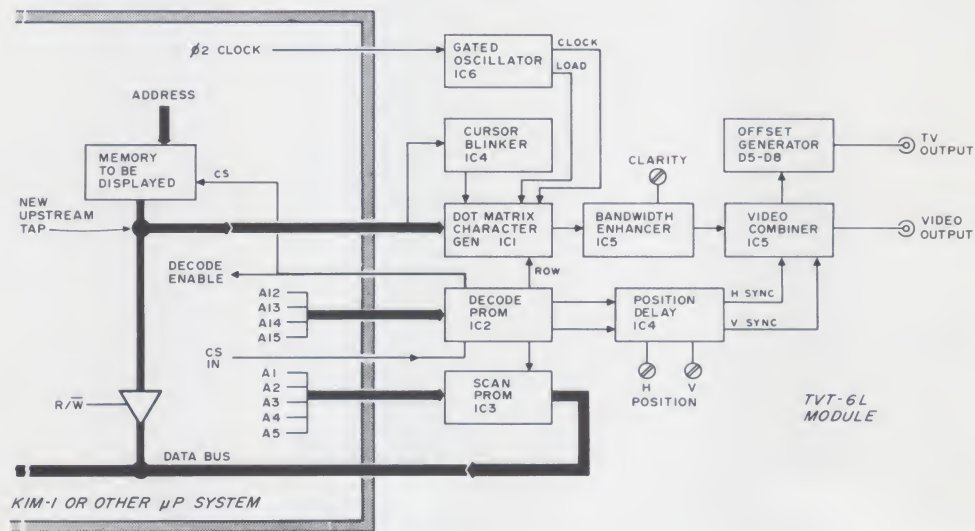


Fig. 1a. TVT-6L Block Diagram. The CPU does all the work.

least for the 16 x 32 display.

Three switches on the TVT-6L let you program the module to suit your particular needs. One switch picks 32 versus 64 character lines when used with suitable scan software. A second switch gives you a choice of no cursor or of a winking underline cursor under software control. The final switch is



Fig. 1b. Data bus definitions.

the neatest one to watch since it gives you a choice of all upper case or mixed upper and lower alphanumerics.

### Scanning

A SCAN program activates the DECODE memory once each horizontal line, which

 


Fig. 4. TVT-6L printed circuit board layout (full size).

results in serial video being output for that particular line. If the program calls for a blank or retrace scan, all zeros are output, resulting in an all-black line. After a horizontal scan, the scan program computes the character and row information needed for

the next line, and continues this way, on through one composite frame of fully interlaced video.

The design of a scan program is extra tricky since you have to control the exact number of microseconds everything takes to keep both

the computer and the TV set happy. But once the scan program is designed and debugged, it's nothing but several dozen words of RAM or ROM available when needed to output the contents of the memory pages as video.

All our scan program does is cause the pages of memory reserved for characters to appear on the screen. *The SCAN program has absolutely nothing to do with how the characters get onto or off of that memory, and couldn't care less.* Your ordinary

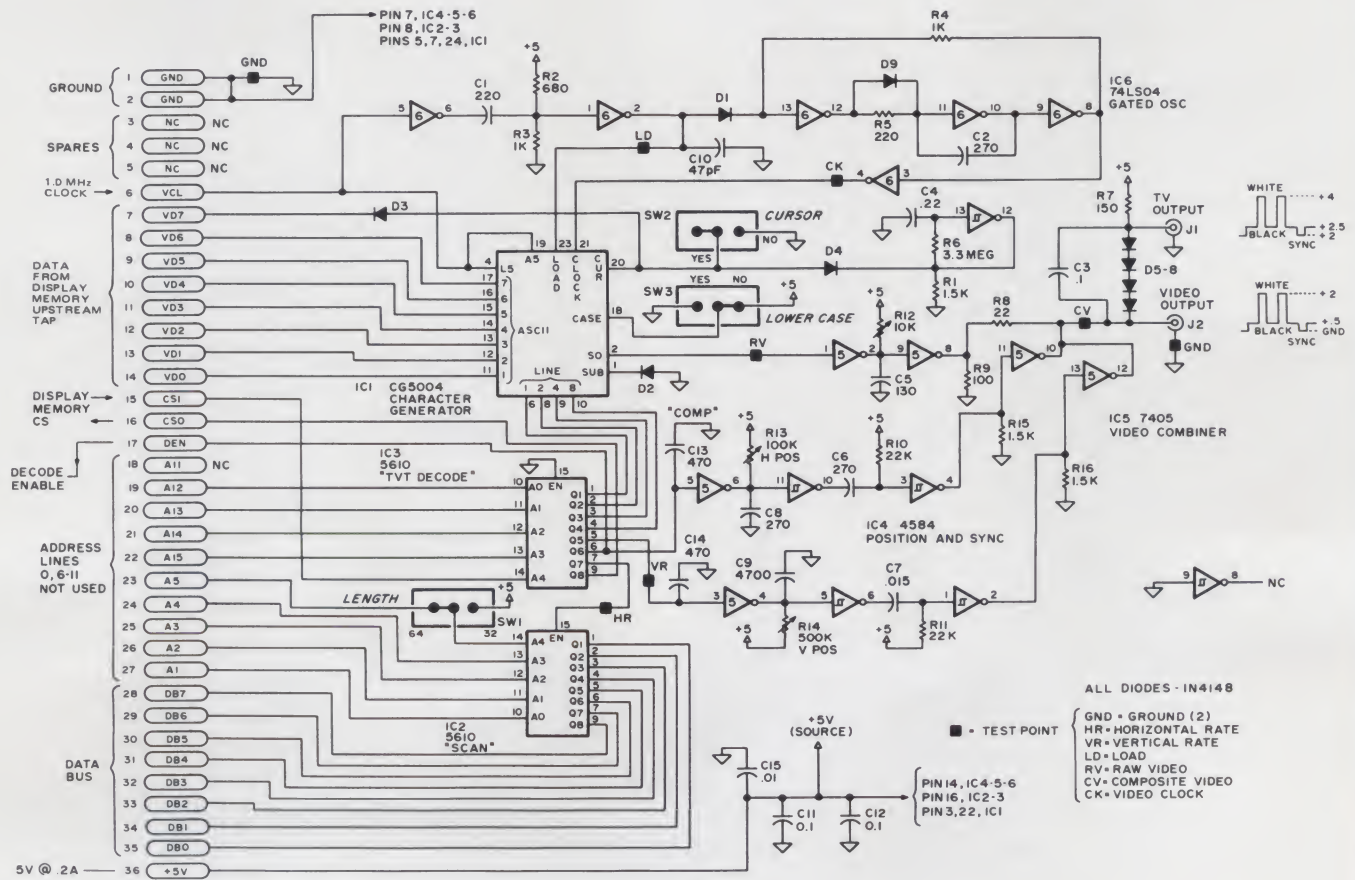


Fig. 2. TVT-6L Schematic.

WORD	NOTES	7	6	5	4	3	2	1	0
0	LDY 240 <sub>B</sub>	00	00	00	00	00	00	00	00
1	" "	00	00	00	00	00	00	00	00
2	" "	00	00	00	00	00	00	00	00
3	" "	00	00	00	00	00	00	00	00
4	" "	00	00	00	00	00	00	00	00
5	" "	00	00	00	00	00	00	00	00
6	" "	00	00	00	00	00	00	00	00
7	" "	00	00	00	00	00	00	00	00
8	" "	00	00	00	00	00	00	00	00
9	" "	00	00	00	00	00	00	00	00
10	" "	00	00	00	00	00	00	00	00
11	" "	00	00	00	00	00	00	00	00
12	" "	00	00	00	00	00	00	00	00
13	" "	00	00	00	00	00	00	00	00
14	" "	00	00	00	00	00	00	00	00
15	" "	00	00	00	00	00	00	00	00
16	" "	00	00	00	00	00	00	00	00
17	" "	00	00	00	00	00	00	00	00
18	" "	00	00	00	00	00	00	00	00
19	" "	00	00	00	00	00	00	00	00
20	" "	00	00	00	00	00	00	00	00
21	" "	00	00	00	00	00	00	00	00
22	" "	00	00	00	00	00	00	00	00
23	" "	00	00	00	00	00	00	00	00
24	" "	00	00	00	00	00	00	00	00
25	" "	00	00	00	00	00	00	00	00
26	" "	00	00	00	00	00	00	00	00
27	" "	00	00	00	00	00	00	00	00
28	" "	00	00	00	00	00	00	00	00
29	" "	00	00	00	00	00	00	00	00
30	" "	00	00	00	00	00	00	00	00
31	RTS 140 <sub>B</sub>	00	00	00	00	00	00	00	00


Fig. 3a. Truth Table for SCAN PROM, IC2.

WORD	NOTES	7	6	5	4	3	2	1	0
0	NORMAL 100	00	00	00	00	00	00	00	00
1	NORMAL 100	00	00	00	00	00	00	00	00
2	BLANK 040	00	00	00	00	00	00	00	00
3	LINE 1 041	00	00	00	00	00	00	00	00
4	LINE 2 042	00	00	00	00	00	00	00	00
5	LINE 3 043	00	00	00	00	00	00	00	00
6	LINE 4 044	00	00	00	00	00	00	00	00
7	LINE 5 045	00	00	00	00	00	00	00	00
8	LINE 6 046	00	00	00	00	00	00	00	00
9	LINE 7 047	00	00	00	00	00	00	00	00
10	LINE 8 050	00	00	00	00	00	00	00	00
11	LINE 9 051	00	00	00	00	00	00	00	00
12	LINE 10 052	00	00	00	00	00	00	00	00
13	LINE 11 053	00	00	00	00	00	00	00	00
14	V SYNC 120	00	00	00	00	00	00	00	00
15	NORMAL 100	00	00	00	00	00	00	00	00
16	NORMAL 300	00	00	00	00	00	00	00	00
17	NORMAL 300	00	00	00	00	00	00	00	00
18	BLANK 040	00	00	00	00	00	00	00	00
19	LINE 1 041	00	00	00	00	00	00	00	00
20	LINE 2 042	00	00	00	00	00	00	00	00
21	LINE 3 043	00	00	00	00	00	00	00	00
22	LINE 4 044	00	00	00	00	00	00	00	00
23	LINE 5 045	00	00	00	00	00	00	00	00
24	LINE 6 046	00	00	00	00	00	00	00	00
25	LINE 7 047	00	00	00	00	00	00	00	00
26	LINE 8 050	00	00	00	00	00	00	00	00
27	LINE 9 051	00	00	00	00	00	00	00	00
28	LINE 10 052	00	00	00	00	00	00	00	00
29	LINE 11 053	00	00	00	00	00	00	00	00
30	V SYNC 320	00	00	00	00	00	00	00	00
31	NORMAL 300	00	00	00	00	00	00	00	00

Fig. 3b. Truth Table for DECODE PROM IC3.

KIM-1 firmware can be used to load and dump memory to cassette tape. Your internal keypad can be used to put messages onto the screen by writing onto the memory pages. This trick gives you a zero cost ASCII keyboard and encoder, but at the hassle of having to write everything in hex rather than ASCII code.

 For most uses, you'll want to add an external ASCII keyboard, entering on parallel A inputs and interrupting the Scan program every time you want to change a character. We'll be looking at a full scrolling cursor program later,



ONE REQ'D--MAKE FROM 1.57MM SINGLE SIDED G-10 PC MAT'L

Fig. 5. Mechanical and drilling details for PC board.

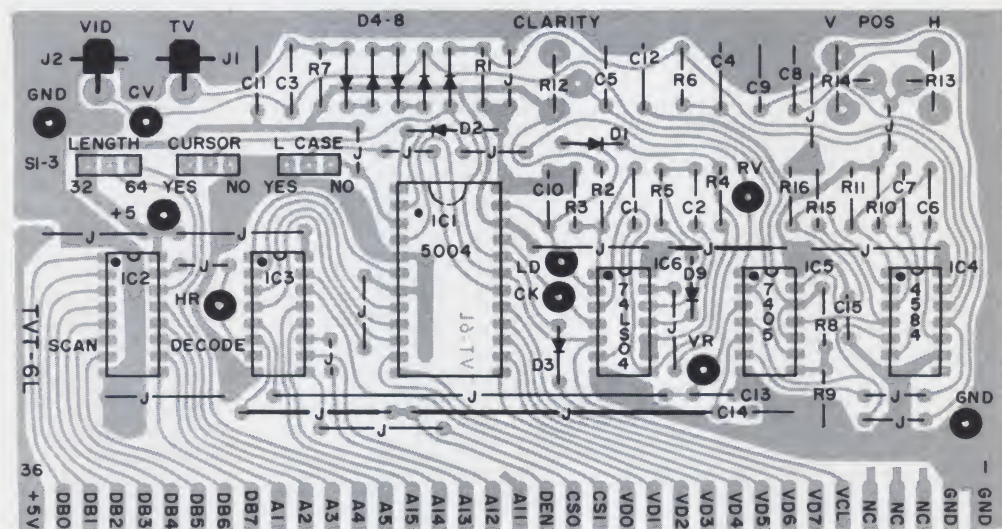


Fig. 6. Components placement overlay.

but the important point now is that you use whatever ordinary KIM-1 compatible programs you like to fill and empty the display memory pages. Your separate Scan program simply puts the memory pages on the screen.

This way, you have total access to the screen memory at any time for any reason. Things like a displayed real time clock are trivial, and you can load and dump characters at a fantastic rate. With a simple Hex-to-ASCII adapter, you can also display op-code

directly instead of alphanumeric characters. Note that this new TVT approach isn't DMA (Direct Memory Access) with its related drivers and access hassles. Your character memory is, looks, feels, and tastes just like any other memory in the microcomputer, since we've kept our upstream tap a secret from the CPU.

#### Building It

Fig. 2 shows you the schematic along with its parts list, while Fig. 3 gives you the

truth tables for the DECODE and SCAN read only memories. Note that these are Tri-state 32 x 8 PROMs. Their programs obviously change if you use a system different from the KIM-1.

You'll find a full size printed circuit layout in Fig. 4, along with the mechanical and drilling details of Fig. 5. Components are located per the overlay of Fig. 6.


Start construction with the jumpers, using sleeving where shown. Follow this up with the nine test points and

C1	220 pF polystyrene
C2, 6, 8	270 pF polystyrene
C4	0.22 uF mylar
C3, 11, 12	0.1 uF mylar (Disks OK for C11, 12)
C5	130 pF polystyrene
C7	.015 uF mylar
C9	.0047 uF mylar
C10	47 pF polystyrene
C13, 14	470 pF disk
C15	.01 uF disk
D1-9	1N4148 or equivalent silicon computer diode. D1, D9 must be quality units.
IC1	CG5004L-1 character Generator IC (STD Microsystems)
IC2	IM5600 or equivalent 32 x 8 Bipolar Tri-state PROM "SCAN"
IC3	IM5600 or equivalent 32 x 8 Bipolar Tri-state PROM "DECODE"
IC4	4584 CMOS Hex Schmitt Trigger (Motorola)
IC5	7405 TTL Hex open collector inverter
IC6	74LS04 LS TTL hex inverter
J1, 2	PC Mount Phono Jack, Keystone 571
R1, 15, 16	1.5k, 1/4 watt carbon film resistor
R2	680 ohm, "
R3, 4	1k, "
R5	220 ohm, "
R6	3.3 Megohm, "
R7	150 ohm, "
R8	22 ohm, "
R9	100 ohm, "
R10, 11	22k, "
R12	10k upright trimmer potentiometer CTS U201 "CLARITY"
R13	100k, " "H POS"
R14	500k, " "V POS"
S1-3	SPDT miniature switch 3.17 mm pin centers
MISC:	PC Board, etched and drilled per Fig. 4; Test Point Terminals (9); PC Sockets, 24 pin (1), 16 pin (2), 14 pin (3); Matching connector (Amphenol 225 or equivalent); Sleeving; jumper material; solder.


NOTE: The following are available from PAIA Electronics, Box 14539, Oklahoma City, OK, 37114:

PC Board, etched and drilled, #TVT-6LB,	\$4.00
Complete kit of all above parts #TVT-6LK,	\$59.95
Assembled and Tested TVT-6L, #TVT-6LAT,	\$75.00
KIM Coded Cassette, #TVT-6LC,	\$5.00

### Complete Parts List, TVT-6L.

 

 (a) DIRECT VIDEO MODS NEEDED FOR SHORTER LINE LENGTHS



(b) ADDITIONAL MODS THAT MAY BE NEEDED FOR 64 CHARACTER LINES

Fig. 7. Mods to TV set are greatly simplified thanks to already offset "TV" output on TVT-6L. DO NOT ATTEMPT DIRECT VIDEO ON A HOT CHASSIS (NO POWER TRANSFORMER) SET!

keyboard on the parallel A inputs and works with any of the display formats by changing the key words as shown. This particular cursor system includes all the bells and whistles, such as full, rapid cursor motions in all directions, scrolling, erase to end of screen, and so on. It takes up most of page 01 in the KIM-1. You can easily make the cursor program longer for super fancy editing or shorter for a minimum sequential loading, per your choice.

### Modifying your KIM

Table II gives you a complete listing of all pinouts on the TVT-6L along with the interface connections needed for either a KIM-1 or KIM-2 interface. The actual computer mods are outlined in Fig. 8. For the KIM-1, you add a connector along the top and make wiring pencil direct connections as shown. The foil is cut in ONE place along the 1K memory chip select line and a changeover switch is added. With the switch in the NORMAL position, the chip select is driven from K0 as usual. In the TVT position, the chip select line is driven from the TVT's CSO line, which is a *negative logic* OR of K0 and the TVT's scan access.


For larger displays, you'll need extra memory. Fig. 8b shows us the modifications for a KIM-2 memory. These mods first convert the KIM-2 decodings so that the KIM-2 works on the second, third, fourth, and fifth "K" of memory, or addresses 0400-13FF. Only addresses 0400 through 0FFF may be used for TVT page storage, although the remaining space is available for other computer use. The rest of the KIM-2 mods are similar to those on the KIM-1.

Even if you are going to use extra memory (who isn't?), convert the KIM-1 anyway as it is the simplest and best way to get started with your video displays. The changeover switch lets you run with the TVT-6L out of

the low profile IC sockets, the switches, and the output phono jacks. Finally, add the resistors, pots, capacitors, and diodes. Be sure to note the polarity of each diode as it is added. Use fine solder and a small iron, and be sure to carefully double-check for any splashes or missed connections.

### Software

Table I shows us some tested and workable KIM software. Program 1-A is the scan program for a 16 x 32 fully interlaced 512 character display that can be moved around as needed. Program 1-B is a dual program that you can set up as 25 x 64 or 13 x 64 fully interlaced displays with larger characters. Finally, Program 1-C gives us a four-in-one full performance scrolling cursor. 1-C accepts an external ASCII

 

Closeup of TVT-6L module. Three of the six! ICs used are hex inverters. Switches give choice of line length, upper and lower case, cursor. Twin jacks give either monitor video or already-translated TV video. Both outputs are enhanced for minimum bandwidth needs. Module is adaptable to many popular microprocessors and microcomputers.


the socket. In one position, the computer works normally; in the other, it will work as a TVT or transparently so long as the TVT is in the socket and so long as memory locations 2000 to EFFF are not called.

### TV Mods

The TV output with its +4 white bias level greatly simplifies your direct video interface. Fig. 7 shows how to "borrow" the headphone jack on a Panasonic T126A and convert it into an automatic video changeover switch. The only new parts needed are two short pieces of miniature coax. The sound trap is defeated by lifting the hot end of the 4.5 Megahertz crystal.

This type of conversion works on any small screen, solid state TRANSFORMER OPERATED portable B and W television set, so long as the set needs a bias voltage around +4 volts at the input to the first video stage.

In order to use the 64 character displays on an ordinary TV without extensive video bandwidth changes, the television's horizontal frequency is run much lower than normal, around 11 kHz. This means that you'll most likely need a width and hold modification for 64 or other long character lines. On the set shown, you can use a coil of 48 turns of #24 wire on a 1.27 cm diameter nylon form in series with the existing

 

The KIM-1 with a difference. Cable at top delivers enhanced video direct to your TV set or monitor.

width coil. A new hold mylar capacitor of one third the normal value, or .022 uF, is added in parallel to C409 to extend the hold range downwards.

Note that the reduced horizontal frequency and reduced width are only needed on 64 character lines. The shorter 32 character lines run at normal horizontal speed. This tradeoff buys us a lot in the way of being able to scan characters with the CPU in the first place and eliminates any need for video bandwidth extension, so it is well worth the simple and reversible mods needed. Clip-

on RF modulators can also be used as shown in the *TV Typewriter Cookbook* and *Microprocessor Based Video Displays*, again thanks to the reduced horizontal rate with long line lengths.


With any TV modification, be sure to have a SAMS photofact on hand and get expert help if you've never done a video input conversion before. NEVER ATTEMPT DIRECT VIDEO INTO A

HOT CHASSIS OR TRANSFORMERLESS TELEVISION SET.

### Initial Checkout

Always have a good oscilloscope on hand for your initial checkout, and always do your first check on a KIM-1 in the 16 x 32 utility scan program 1A mode. Don't worry about doing anything initially except displaying code that already happens

 
1. Add a new 36 pin, single readout connector along the top of the KIM-1 above the crystal. Small "L" brackets can be added to use existing holes.
  2. Make short and direct wire connections as shown in Table II. Use a wiring pencil for all connections *except* +5 and GND, which should be short lengths of #18 wire.
- Do not use ribbon cable or attempt extending the TVT-6L.*
3. Break ONE foil run as shown, and add a DPDT changeover switch:



With the switch in the TVT position, operation is totally transparent so long as the TVT-6L is in its socket and addresses 2000-EFFF aren't called.

Fig. 8a. Modifying your KIM-1 for the TVT-6L.

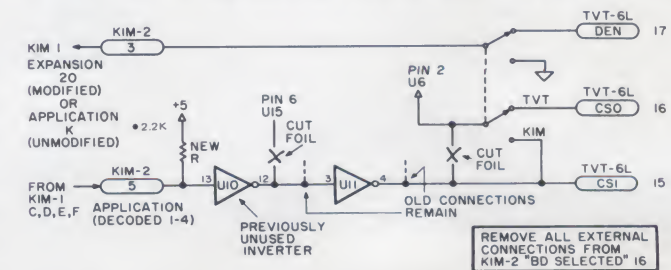1. Add a new 36 pin, single readout connector along the left edge of the card, the side away from the regulator. Small "L" brackets can use existing holes if one of the handle eyelets is replaced with a #6 screw.
2. Make short and direct wire connections as shown in Table II. Use a wiring pencil for all connections *except* +5 and GND.
3. Break TWO foil leads as shown, and add a DPDT changeover switch:



Note that we now have a new input pin on Connector 5 that is driven by KIM-1 decodings K1, 2, 3, and 4 in parallel from Application connector C, D, E, and F.

We also have a new output pin on Connector 3 that provides a ground for the KIM-1 Decode Enable. This is connected to Application Connector K on an *unmodified* KIM-1 and to Expansion Connector 20 or a KIM-1 modified per Fig. 8a.

Note further that BD SELECTED output Connector 16 is not used. These modifications cause your KIM-2 to respond to addresses 0400-13FF. The program address switches are no longer used.

Fig. 8b. Modifying your KIM-2 for the TVT-6L.

to be on pages 02 and 03.

Center the three controls, switch to "32", cursor OFF and Lower Case OFF, plug the TVT-6L into your KIM-1, insert IC2 and IC3 *only*, and apply power. Go through the usual initialization, putting the KIM-1 in its binary mode with the interrupt returning you to keyboard operation. Then, try to operate the KIM-1 with a simple program on page zero to make sure the chip select and decode enable logic on the TVT-6L is passing things through properly and transparently.

Now, check address 2000 with your keyboard monitor. It should contain an A0. *If it doesn't, stop immediately and find out why!* Check the next 29 locations for more A0s followed by two 60s followed by another string of 30 A0s and so on. You should now be able to write and single step a simple program that will transfer control from KIM to TVT back to KIM again (see Example 1).

Your KIM-1 should start at 0000, jump to 2000, index sixteen times by twos to 201E, return to 0003 and stick there in the trap. *Don't go on till the KIM and TVT can pass control back and forth to each other.*

Next, add IC6 and check testpoints LD and CK with a decent scope. The waveforms should look exactly like Fig. 9. In particular, they should be clean and stable. The clock should have eight narrow positive clock pulses between load commands. *Do not omit checking these waveforms.*

Add the rest of the ICs,

 


Fig. 9. Key high frequency waveforms. Clock "CK" must be clean, jitter free, and have narrow positive duty cycle shown.

0000	JSR	20	00	20	Go to TVT
0003	JMP	4C	03	00	Trap

Example 1.

Table I. Some software.

A. Program for a 16 line, 32 character per line Interlaced TVT-6L Raster Scan:

uP — 6502      Start — JMP 17A6      Displayed 0200-03FF  
System — KIM-1      End — Interrupt      Program Space 1780-17d4

Upper Address (178A0)								Lower Address (1789)								
*	*	*	*	0	0	1	V8	V4	V2	V1	H16	H8	H4	H2	H1	
0, 1, F	— normal program (no tvt)															
2	— blank scan															
3	— scan row 1															
4	— scan row 2															
.. (etc)	.....															
d	— scan row 11															
E	— vertical sync pulse															
1780	CLC	18														Clear Carry
1781	STA	8d	(8A)	(17)												Store Upper Address
1784	PHA	48														Equalize 10 microseconds
1785	PLA	68														continued
1786	BNE	d0	00													continued
1788	JSR	20	00	20												///Character Scans 0-11///
178b	ADC	69	10													Increment Character Scan Counter
178d	CMP	C9	E0													Character Scan Counter Overflow?
178F	BCC	90	F0*													No. Scan next row of character
1791	TAX	AA														Save Upper Address
1792	LDA	Ad	(89)	(17)												Get Lower Address
1795	ADC	69	1F													Increment Lower Address; Save carry
1797	STA	8d	(89)	(17)												Restore Lower Address; Save carry
179a	TXA	8A														Get Upper Address
179b	ADC	69	40													Reset Upper Address; add carry
179d	BNE	d0	00													Equalize 3 microseconds
179F	JSR	20	04	20												///Blank Character Scan 12///
17A2	CMP	C9	24													Is it the "17th" row of characters?
17A4	BCC	90	dA*													No, start a new row of characters
17A6	LDA	A5	(EC)													Get Interlace Word
17A8	ADC	69	7F													Change Field via Carry bit
17AA	BCS	B0	05*													Jump if Even Field
17AC	STA	8d	(EC)	E0												Odd Field V Sync; Restore Interlace
17Af	LDX	A2	36													Load Odd (short) # of blank scans
17b1	LDY	A0	05													Equalize 31 microseconds
17b3	DEY	88														continued
17b4	BPL	10	Fd*													continued
17b6	BCC	90	05*													Jump if odd field
17b8	STA	8d	(EC)	E0												Even Field V Sync; Restore Interlace
17bb	LDX	A2	37													load Even (long) # of blank scans
17bd	JSR	20	1E	20												///1st V Blanking scan///
17C0	PHA	48														Equalize 9 Microseconds
17C1	PLA	68														continued
17C2	CLD	d8														continued
17C3	LDA	A9	00													Initialize Lower Address
17C5	STA	8d	(89)	(17)												continued
17C8	LDA	A9	22													Initialize Upper Address
17CA	STA	8d	(8A)	(17)												continued
17Cd	JSR	20	00	20												///Rest of V Blanking scans///
17d0	DEX	CA														One less scan
17d1	BMI	30	Ad*													Start Character Scan
17d3	BPL	10	Ed*													Repeat V Blanking Scan

NOTES: TVT-6L must be connected and both the SCAN and DECODE PROMs must be in circuit for program to run.

Both 17AC and 17b8 require that page 00 be enabled when page E0 is addressed. This is done automatically in the KIM-1 decode circuitry.

Location 00EC on page zero is reserved as an interlace storage bit.

Step 1788 goes to where the upper address stored in 178A and the lower address stored in 1789 tells it to. Values in these slots continuously change throughout the program.

For a 525 line system, use 17b0 34 and 17bC 35 and a KIM-1 crystal of 992.250 kHz. This is ONLY needed for a video superposition or tilting applications; the stock 1 MHz





17C9	LDA	A9	3b		Initialize Odd Character End Compare
17Cb	STA	8d	(A0)	(17)	continued
17CE	JSR	20	3F	20	///1st V Blanking Scan////
17d1	LDA	A9	C0		Initialize Lower Address
17d3	STA	8d	(87)	(17)	continued
17d6	BMI	30	00		Equalize 3 microseconds
17d8	CLD	d8			Equalize 4 microseconds
17d9	NOP	EA			continued
17dA	JSR	20	00	20	///Rest of V Blanking Scans///
17dd	DEX	CA			One Less Scan
17dE	BMI	30	A0*		Start Character Scan
17E0	CLC	18			Clear Carry
17E1	BPL	10	F5*		Repeat V Blanking Scan

NOTES: TVT-6L must be connected and both the SCAN and DECODE PROMS must be in circuit for program to run.

Both 17A9 and 17bF require that page 00 be enabled when page E0 is addressed. This is done automatically in the KIM-1 decode circuitry.

Location 00EC on page zero is reserved as an interlace storage bit.

Step 1786 goes to where the upper address stored in 1788 and the lower address stored in 1787 tells it to. Values in these slots continuously change throughout the program.

Values in slots 1781 (Upper address start) and 17A0 (Character end compare) alternate with the field being scanned.

Horizontal Scan Frequency = 11.494 kHz. Vertical frequency = 60.0222 Hertz. 87 microseconds per line 191.5 lines per field; 2 fields per frame, 383 lines total.


TVT-6L switch must be in the "64" position.

( ) Denotes an absolute address that is program location sensitive.

\* Denotes a relative branch that is program length sensitive.

Program may be used for 13 x 64 large characters or 25 x 64 small characters by changing the following slots:

	13 x 64	25 x 64
178A	10	20
17Ad	14	0E
17Af	24	24
17b4	28	2b
17C3	15	0F
17C5	24	34
17CA	28	3b

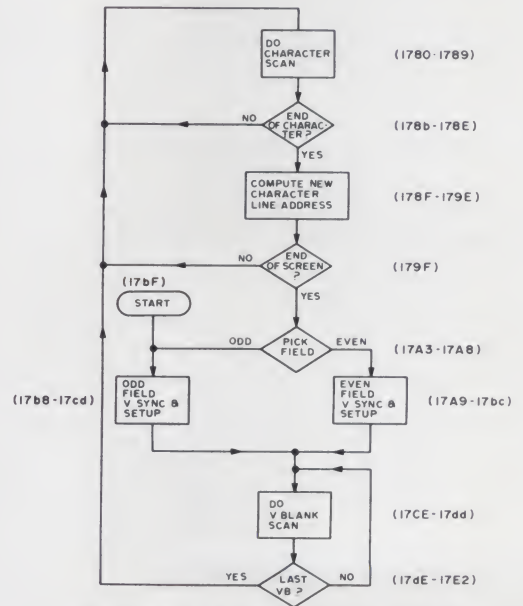


FLOWCHART 13 X 64 OR 25 X 64 INTERLACED SCAN NO 68

C. Program for a Four-in-One full performance Scrolling Cursor:

uP - 6502      Start -  $\overline{\text{IRQ}}$       Program Space 0100-01dF  
 System - Kim 1,2      End - RTI      + Two words page zero (ED,EF)

Input to parallel Word A

 

- |                           |  |
|---------------------------|--|
| Clear - CAN (18)          | Cursor Right - HT (09)                               |
| Carriage Return - CR (0d) | Cursor Home - SOH (0A)                               |
| Cursor Up - VT (0b)       | Scroll Up - DC1 (11)                                 |
| Cursor Down - LF (0A)     | Erase To End - ETX (03)                              |
| Cursor Left - BS (08)     | Enter -- all characters and all unused CTRL commands |

Address	Instruction	Op Code	Mode	Comments	
Enter via IRQ					
0100	PHA	48		Save A	
0101	LDY	A0	00	Reset Y Index	
0103	LDA	A5	(EE)	Get Cursor and test for range	
0105	CMP	C9	04	Is cursor below maximum?	
0147	0107	BCS	b0 3E*	No, Home Cursor	
	0109	CMP	C9 02	Is cursor above minimum?	
0147	010b	BCC	90 3A*	No, Home cursor	
	010d	LDA	b1 (Ed)	Get Old Cursed character	
010F	AND	29	7F	Erase Old Cursor	
0111	STA	91	(Ed)	Replace character without cursor	
0113	LDA	Ad	00	Get New character from A parallel Int.	
0116	CMP	C9	20	Is it a character to be entered?	
013E	0118	BCS	b0 24*	Yes, go and enter character	
	011A	CMP	C9 18	Clear Screen?	
015E	011C	BEQ	F0 30*	Yes, go clear screen	
	011E	CMP	C9 0d	Return carriage?	
0152	0120	BEQ	F0 30*	Yes, go return carriage	
	0122	CMP	C9 0b	Move cursor up?	
0194	0124	BEQ	F0 6E*	Yes, move cursor up	
	0126	CMP	C9 0A	Move Cursor down?	
0166	0128	BEQ	F0 3C*	Yes, move cursor down	
	012A	CMP	C9 09	Move cursor right?	
0158	012C	BEQ	F0 2A*	Yes, move cursor right	
	012E	CMP	C9 08	Move Cursor left?	
01A7	0130	BEQ	F0 75*	Yes, Move cursor to left	
	0132	CMP	C9 01	Home Cursor?	
0147	0134	BEQ	F0 11*	Yes, Home cursor	
	0136	CMP	C9 11	Scroll Up?	
0175	0138	BEQ	F0 3b*	Yes, Scroll Up	
	013A	CMP	C9 03	Erase to End of Screen?	
01b1	013C	BEQ	F0 73*	Yes, Erase to End of Screen	
	013E	CLD	d8	Assure Hex arithmetic mode	
013F	JSR	20	(d3)	(01) ////Enter Character via Sub////	
0142	BNE	d0	06*	Did Screen Overflow?	
0144	JMP	4C	(75)	(01) Select Scroll or Wraparound	
0147	JSR	20	(C2)	(01) ////Home cursor via sub////	
014A	LDA	b1	(Ed)	////Restore Cursor////	
014C	ORA	09	80	Add Cursor to cursed character	
014E	STA	91	(Ed)	Restore cursed character	
0150	PLA	68		Restore Accumulator	
OUT	0151	RTI	40	Return to Scan	
	0152	LDA	A5	////Carriage Return////(get cursor)	
	0154	ORA	09	1F	Move cursor all the way right
	0156	STA	85	(Ed)	Restore Cursor
0142	0158	JSR	20	(d5)	(01) Increment cursor
	015b	JMP	4C	(42)	(01) Scroll or wraparound if needed; finish
	015E	JSR	20	(C2)	(01) ////Clear////(home cursor)
	0161	JSR	20	(Cb)	(01) clear screen via subroutine
0147	0164	BEQ	F0 E1*	Finish	
	0166	LDA	A5	(Ed)	////Cursor Down////(get cursor)
	0168	CLC	18		Clear Carry
	0169	ADC	69	20	Move cursor down one line
0142	016b	STA	85	(Ed)	Restore Cursor
	016d	BCC	90	03*	Overflow of page?
	016F	JSR	20	(d9)	(01) Yes, increment next higher page
	0172	JMP	4C	(d2)	(01) Scroll or wraparound if needed; finish
0142	0175	JSR	20	(C2)	(01) ////Scroll Up////(home cursor)
	0178	LDY	A0	20	Add offset to index
	017A	LDA	b1	(Ed)	Get offset indexed character
	017C	LDY	A0	00	Remove offset from index
	017E	JSR	20	(d3)	(01) Enter moved character and increment
	0181	BNE	d0	F5*	Repeat?
	0183	CLC	18		Clear Carry
	0184	LDA	A9	03	Set A to page of last line
	0186	STA	85	(EE)	Set Cursor to page of last line
	0188	LDA	A9	E0	Load A to start of last line
014A	018A	STA	85	(Ed)	Set Cursor to start of last line
	018C	BCS	b0	bC*	Finish if carry set
0184	018E	JSR	20	(Cb)	(01) Clear last line
	0191	SEC	38		Set Carry
	0192	BCS	b0	F0*	Restore cursor to start of last line
	0194	LDA	A5	(Ed)	////Cursor Up////(get cursor)
014A	0196	SEC	38		Set Carry
	0197	SBC	E9	20	Move Up one line
	0199	STA	85	(Ed)	Restore Cursor
	019b	BCS	b0	Ad*	Underflow of page?
	019d	DEC	C6	(EE)	Yes, Decrement page
	019F	LDA	A9	01	Set A to page below home page
	01A1	CMP	C5	(EE)	Did screen underflow?
014A	01A3	BNE	d0	A5*	No, Finish

load program 1A, switch to single step off, jump to 17A6 and hit GO. Your first check should be that the program *will* run, returning to the keyboard monitor when you hit stop and picking up on go again. Addresses should always be within the program bounds of being somewhere between 2000 and EFFF or somewhere between 1780 and 17d3.

Check test point VR for a one microsecond pulse every 16.7 milliseconds. If your scope has trouble with low duty cycle waveforms, you can try pin 6 of IC4, which should be a one millisecond or so pulse every 16.7 milliseconds. For the acid test, switch to *line* sync. This pulse is your vertical sync pulse. It should wander around *very* slowly with respect to the power line sync. This pulse is created both by the hardware and your SCAN program. *Stop right here till you have it there and stable.*

Now, plug in your fully modified TV or monitor to the VID output, or else a Fig. 8 modified TV to the TV output. You should have a random but stable display of characters, along with some weird control symbols. Position them and sharpen them with the controls. The CLARITY control makes the characters brighter in one direction and sharper in the other — pick what you like. At this point you should have a stable and attractive display. Use *minimum* contrast for sharpest characters.

The rest should be downhill all the way. Check the LCASE switch and the CURSOR switch. Around half the characters should wink cursors at you, since the cursor recognizes any bit eight set as a cursor and since you have a random page load, rather than a page of characters with a single cursor location.

If everything checks out so far, you can now go on to longer character lines, external keyboards, cursor loading (don't forget to load the TRO

0147	01A5	BEQ	F0	A0*	Yes, Home cursor
	01A7	DEC	C6	(Ed)	/// <i>Cursor Left</i> /// <i>(decrement cursor)</i>
	01A9	LDA	A9	FF	Set A to page underflow
	01Ab	CMP	C5	(Ed)	Test for page underflow
019d	01Ad	BEQ	F0	(EE)	Change page if off page
014A	01AF	BNE	d0	99*	Finish if on page
	01b1	LDA	A5	(EE)	/// <i>Erase to EOS</i> /// <i>(get cursor)</i>
	01b3	PHA	48		Save Upper Cursor location on stack
	01b4	LDA	A5	(Ed)	Get Lower Cursor location
	01b6	PHA	48		Save Lower Cursor location on stack
	01b7	JSR	20	(Cb)	(01) Clear to End of Screen
	01bA	PLA	68		Get lower cursor location off stack
	01bb	STA	85	(Ed)	Restore lower cursor
	01bd	PLA	68		Get upper cursor location off stack
	01bE	STA	85	(EE)	Restore upper cursor
014A	01C0	BNE	d0	88*	Finish
	01C2	LDA	A9	00	/// <i>Subroutine-HOME CURSOR</i> /// <i>///</i>
	01C4	STA	85	(Ed)	Set lower cursor to home value
	01C6	LDA	A9	02	Load A with home page value
	01C8	STA	85	(EE)	Set upper cursor to home page
	01CA	RTS	60		Return to main cursor program
	01Cb	LDA	A9	20	/// <i>Subroutine-ENTER SPACES</i> /// <i>///</i>
	01Cd	JSR	20	(d3)	(01) Enter space via character entry sub
	01d0	BNE	d0	F9*	Repeat if not to end of screen
	01d2	RTS	60		Return to main cursor program
	01d3	STA	91	(Ed)	/// <i>Subroutine-ENTER AND INCREMENT</i> /// <i>///</i>
	01d5	INC	E6	(Ed)	Enter character and increment
	01d7	BNE	d0	06*	Overflow of page?
	01d9	INC	E6	(EE)	Yes, Increment cursor page
	01db	LDA	A9	04	Load A with page above display
	01dd	CMP	C5	(EE)	Test for Overflow
	01dF	RTS	60		Return to main cursor program

vector!), and so on, but don't try too much at once. *Always* get the utility 512 character basic display up on a KIM-1 before trying anything fancy. Thanks to the total software control, once you *are* up and working and confident, there's practically no limit to how fancy you get with your display.

More details on all this will appear in *Microprocessor Based Video Displays*, along with such options as a Hex-ASCII converter that displays *Super Front Panel Op-Code* (your whole program at once - how's that for a debug aide?); color graphics options, use of different character generators, different micro-processors, and so on. Watch for it. ■

NOTES: For auto-scrolling use 0145 75. For wraparound, use 0145 47.

*IRQ* vector must be stored in 17FE 00 and 17FF 01.

Total available stack length is 32 words. Approximately 16 are used by operating system, cursor, and scan program. Stack must be initialized to 01FF as is done in KIM operating system. For 30 additional stack locations, relocate subroutines starting at 01C2 elsewhere. For total stack availability, relocate entire program elsewhere.

To protect page, load 00F1 04. To enable entry, load 00F1 00

Cursor address is stored at 00Ed low and 00EE high on page zero.


To display cursor, load 014d 80. To not display cursor, load 014d 00

\* Denotes a relative branch that is program length sensitive

( ) Denotes an absolute address that is program location sensitive

To match this program to the scan program, change the following slots:

	16 x 32 KIM1 0200-03FF	16 x 32 KIM2 0400-05FF	13 x 64 KIM2 04C0-07FF	25 x 64 KIM2 04C0-0AFF
0106	04	06	08	0b
010A	02	04	04	04
0155	1F	1F	3F	3F
016A	20	20	40	40
0179	20	20	40	40
0185	03	05	07	0A
0189	E0	E0	C0	C0
0198	20	20	40	40
01A0	01	03	03	03
01C3	00	00	C0	C0
01C7	02	04	04	04
01dC	04	06	08	0b

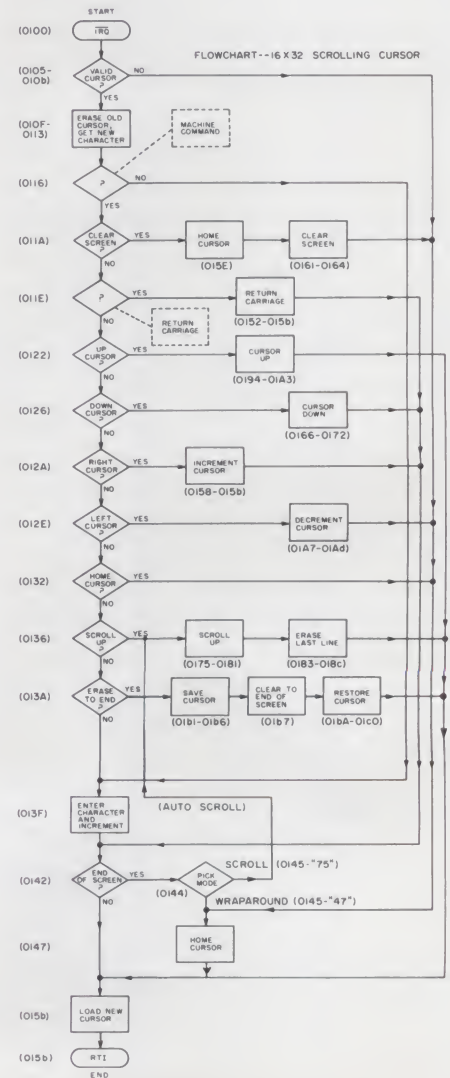

Pin	Ident	Function	Load	8-A KIM-1 Connections	8-B KIM-2 Connections
1, 2*	GND	Ground Return — Heavy foil or wire	—	Expansion 22	Connector 1
3, 4, 5	NC	No Connection — reserved	—	—	—
6*	VCL	Video Clock $\emptyset 2$	1 LSTTL	Expansion U	Pin 4 of U10
7	VD7	Cursor from Display memory	1 LSTTL	Pin 12 of U5	Pin 2 of U3
8	VD6	ASCII Bit 7 from Display memory	1 NMOS	Pin 12 of U6	Pin 6 of U3
9	VD5	ASCII Bit 6 from Display memory	1 NMOS	Pin 12 of U7	Pin 10 of U2
10	VD4	ASCII Bit 5 from Display memory	1 NMOS	Pin 12 of U8	Pin 2 of U2
11	VD3	ASCII Bit 4 from Display memory	1 NMOS	Pin 12 of U9	Pin 6 of U2
12	VD2	ASCII Bit 3 from Display memory	1 NMOS	Pin 12 of U10	Pin 10 of U1
13	VD1	ASCII Bit 2 from Display memory	1 NMOS	Pin 12 of U11	Pin 2 of U1
14	VD0	ASCII Bit 1 from Display memory	1 NMOS	Pin 12 of U12	Pin 6 of U1
15*	CSI	Chip Select <i>from</i> Enable Decoding	1 LSTTL	Pin 1 of U4	Pin 4 of U11
16*	CSO	Chip Select <i>to</i> Display Memory	TTL Out	Pin 13 of U5-U12	Pin 2 of U6
17*	DEN	Decode Enable <i>to</i> KIM	TTL Out	Pin 12 of U4	Connector 3
18	A11	No Connection — reserved	—	—	—
19	A12	Address Line 12	1 LSTTL	Expansion P	Connector R
20	A13	Address Line 13	1 LSTTL	Expansion R	Connector S
21	A14	Address Line 14	1 LSTTL	Expansion S	Connector T
22	AB15	Address Line 15	1 LSTTL	Expansion T	Connector U
23	A5	Address Line 5	1 LSTTL	Expansion F	Connector H
24	A4	Address Line 4	1 LSTTL	Expansion E	Connector F
25	A3	Address Line 3	1 LSTTL	Expansion D	Connector E
26	A2	Address Line 2	1 LSTTL	Expansion C	Connector D
27*	A1	Address Line 1	1 LSTTL	Expansion B	Connector C
28	DB7	Data Bus 7	TTL TS Out	Expansion 8	Connector 8
29	DB6	Data Bus 6	TTL TS Out	Expansion 9	Connector 9
30	DB5	Data Bus 5	TTL TS Out	Expansion 10	Connector 10
31	DB4	Data Bus 4	TTL TS Out	Expansion 11	Connector 11
32	DB3	Data Bus 3	TTL TS Out	Expansion 12	Connector 12
33	DB2	Data Bus 2	TTL TS Out	Expansion 13	Connector 13
34	DB1	Data Bus 1	TTL TS Out	Expansion 14	Connector 14
35	DB0	Data Bus 0	TTL TS Out	Expansion 15	Connector 15
36*	+5V	+5 Volt Supply	200 ma	Expansion 21	Connector Y

NOTES: (See \* Above)

- Pins 1, 2 — Ground should be heavy foil or #18 wire — all other connections are wire pencil short leads. *Do not use ribbon cables or attempt extension.*
- Pin 6 — Video clock must load character generator only when data output is stable and valid. Clock  $\emptyset 2$  on the KIM.
- Pins 15, 16 — Chip select line from decoding to display memory is broken by cutting the foil and then replaced with a negative logic OR (positive AND) of the original chip select and the TVT chip select. *See Figure 8b.*
- Pin 17 — Decode Enable output goes low when TVT is *not* scanning; goes high otherwise. Decoding must be disabled during active scans to allow SCAN memory access to data buss. *See Figure 8b.*
- Pin 27 — Address line A0 is not used in the TVT module as the SCAN memory indexes every *second* microsecond. A0 is used in the display memory addressing.
- Pin 36 — +5 power borrowed from computer. Extra noise on the +5 line will cause skewed or awkward characters; may be fixed usually with extra bypassing. Use heavy foil or #18 wire.

Table II. TVT-6L Interface.