



BUILD  
THE

## AMLIGNER

By DON LANCASTER

... A MULTIPURPOSE  
TUBELESS, TRANSISTORLESS, CORDLESS BC-BAND SIGNAL  
GENERATOR FOR THE RADIO AFICIONADO

**A** BROADCAST-BAND AM signal generator without test cables or even a line cord? Yes! And what's more, it uses no tubes, no transistors, no integrated circuits . . . nothing but a diode, a resistor, a coil, and a couple of capacitors.

Yet, here's an r.f. signal generator that you can use to signal-trace radio receiver troubles, to align the receiver i.f. and front end—provided you first calibrate the unit—and which, in conjunction with any broadcast-band receiver, can be used as a code-practice oscillator by merely substituting the on-

off switch for an ordinary telegraph key.

And what's the miracle ingredient that makes all this possible? Nothing more than a low-power, short-range radio transmitter that sends out an r.f. carrier modulated by a 800-hertz tone signal which is picked up by a receiver placed about eight feet away. We call it, affectionately, the "AMLIGNER." You can build it for about \$7.00.

**How It Works.** The AMLIGNER (Fig. 1) is basically a free-running relaxation oscillator operating at 800 hertz. The circuit is powered by a 22.5-volt battery,


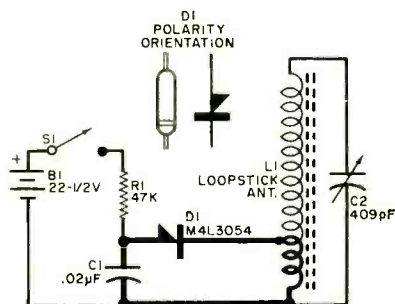


Fig. 1 The AMLIGNER is a free-running relaxation oscillator whose frequency is determined essentially by the value chosen for charging capacitor C1.
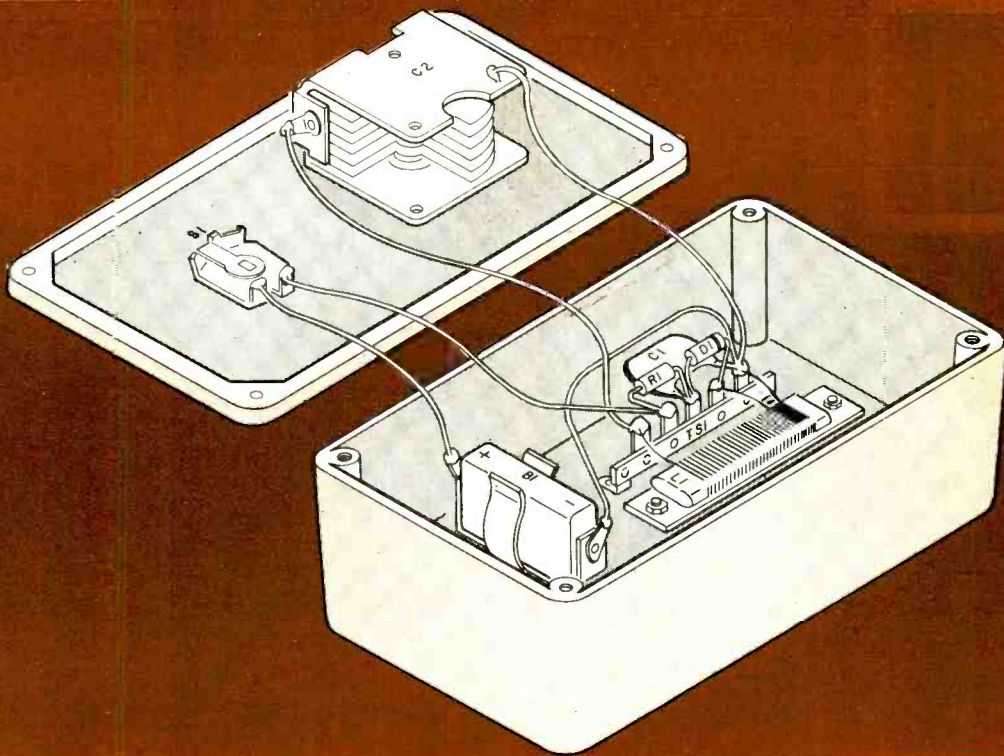
### PARTS LIST

- B1—22½-volt battery
- C1—0.02-µF, 50-volt Mylar capacitor
- C2—15 to 409 pF TRF variable capacitor (similar to Allied Radio 43 A 3524)
- D1—Motorola M4L3054 four-layer diode (available from Allied Radio, Chicago, Ill.)
- LI—Loopstick antenna (similar to J. W. Miller Company 2004)
- R1—47,000-ohm, ½-watt resistor, ± 10%
- S1—S.p.s.t. rotary switch
- I—Plastic case and cover (similar to Harry Davies 240 and 241, or Allied Radio 42 D 7885 and 42 D 7887, respectively)
- Misc.—¾" and 1¾" plastic knobs, #6 hardware or pop rivets, battery holder, 5-pin terminal strip, wire, solder, etc.



Housed in a plastic instrument case, the AMLIGNER can be assembled and wired in a matter of minutes. When wiring components to the terminal strip, be sure to observe polarity orientation of diode D1.

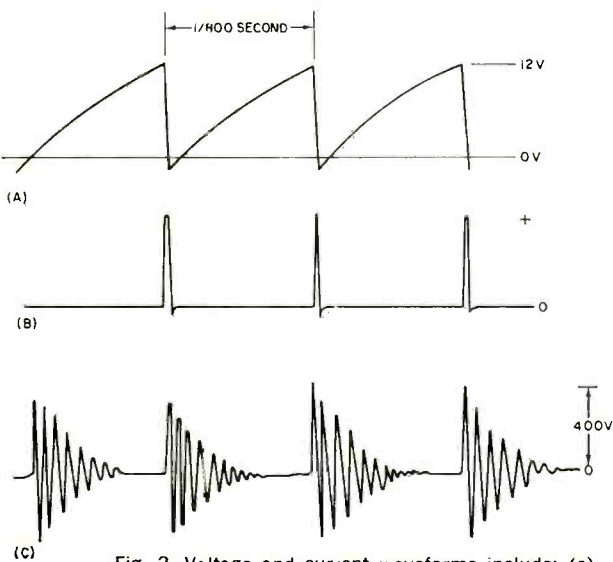


Fig. 2. Voltage and current waveforms include: (a) sawtooth voltage across C1; (b) a current pulse through D1; and (c) a ringing waveform across C2.

which is in series with switch S1, limiting resistor R1, and capacitor C1, shunted by D1 and the primary of L1, a loopstick antenna. The "heart" of the circuit is D1, a four-layer diode which snaps on with a 12-volt forward bias and snaps off when the current through it drops below 1 milliampere.

With S1 closed, C1 begins to charge through R1. When the capacitor charge reaches 12 volts, D1 avalanches and the capacitor discharges through the primary of L1. With C1 discharged, D1 turns off and does not turn on again until C1 recharges to 12 volts. This on-off cycle occurs at a rate of 800 times a second, producing a sawtooth voltage waveform as shown in Fig. 2(a). The waveform of the current through D1 is shown in Fig. 2(b).

As D1 turns off, the sudden decrease of current sets up an oscillating current of a few hundred microseconds duration, and at the natural resonant frequency of the C2-L1 tank circuit, producing the ringing waveform shown in Fig. 2(c).

(Continued on page 99)

## THE AMLIGNER

(Continued from page 61)

Also, the discharge of *C1* through the primary of *L1* induces a rapidly changing voltage in the coil. This voltage is stepped up by transformer action, placing a potential of several hundred volts across tuning capacitor *C2*.

Adjustment of capacitor *C2* determines the frequency of the r.f., carrier which is independent of battery voltage. Since *L1* is an antenna as well as a transformer, it radiates an r.f. energy that can be picked up on any nearby broadcast receiver. The power radiated is well within the limits allowed by FCC regulations.

**Construction.** The circuit must be housed in a non-metallic box. A plastic instrument case is just about ideal for this purpose, but you could use a Masonite or wooden case. Simply follow the pictorial diagram (p. 61). Be sure to keep the leads on *C1*, *D1*, and the primary of *L1* as short as possible to prevent ex-

cessive signal losses in the middle of the band. And, of course, observe polarity when hooking up the battery and diode.

The circuit should perform well with just about any loopstick you care to use, but you'll no doubt encounter performance variations from loopstick to loopstick. The one in the Parts List is quite suitable for this application. You'll also find some performance variations in tuning capacitors, requiring that you custom-calibrate your own dialplate against the frequencies of local radio stations, or with the aid of a signal generator.

**Operating Hints.** When using the AMLIGNER, place it as far away from the receiver as you can so that it will operate on the weakest signal possible. This procedure will insure sharp tuning.

For best results when making oscillator tracking adjustments or car radio antenna trimmer adjustments, always use frequencies at the high end of the dial (around 1600 kHz). Before attempting to adjust the receiver i.f., make certain the AMLIGNER has been properly calibrated for the desired i.f. —50—



The only  
Theatre Organ  
available in kit form  
—for only \$1350.

Build it yourself and  
save over 50%

**Combination Action** Ten buttons select preset combinations of stops — actually move the stop tablets as in pipe organs.

**Percussion** Eight percussion stops provide exciting realism. Celesta, harpsichord, piano, mandolin, xylophone, chrysoglott, orchestral bells, single or reiterating, are played just like the real thing — and sound that way — alone or along with regular organ stops.

**Free Information.** Send today for your copy of Schober's 16-page full-color booklet — plus free 7" recording.

You've asked for it and here it is — the NEW Schober THEATRE ORGAN that you assemble yourself. For the first time in kit form, a real Theatre Organ with that rich, full, old time theatre pipe organ sound. You create the organ, then you create the music!

The Theatre Organ features special voicing, curved console design, two 61-note keyboards, 2-octave radiating pedal clavier, 8 octaves of tone distributed over 5 pitch registers (including a 1-foot register), 35 speaking organ stops, 8 realistic percussion stops, 4 couplers, and vibrato tablet — 48 tablets in all. And all at a truly remarkable low price... you save over \$1,500 (well over 50%) from comparable theatre organs.

Just follow easy step-by-step instructions written in everyday language which anyone can understand. You'll have an unequaled pride when you're finished that only can come from assembling it yourself.

The Theatre Organ starts at \$1,350. This price includes a beautiful walnut console or you can save further by building your own from plans. Options available include combination action, genuine reverberation, percussion, and amplifiers and speakers.

THE Schober Organ CORPORATION

43 West 61st Street, New York, N.Y. 10023

The Schober Organ Corp., Dept. PE-22  
43 West 61st St., New York, N. Y. 10023

- Please send me Schober Organ Catalog and FREE 7-inch "sample" record.
- Enclosed please find \$2.00 for 12-inch quality LP record of Schober Organ music. (\$2.00 refunded with purchase of first kit.)

Name.....

Address.....

City.....State.....Zip No.....

CIRCLE NO. 31 ON READER SERVICE PAGE