

Get the exact time on your TV screen without interfering with the picture

Put the **TIME** on your TV screen



MANY RADIO-ELECTRONICS READERS HAVE asked for a way to connect their Superclock II (R-E, July and August '72) or other digital clocks to their TV set, so they can display time directly on top of an existing TV program. This eliminates the high cost of the self-decoding LED readouts from your Superclock design and is the ultimate in convenience for the discriminating TV viewer. When and if it is approved, the NBS (National Bureau of Standards) TV timing system is a natural source of self-resetting, always accurate signals for your Superclock, and the Revideo unit is the ideal output display.

You can also use the unit to transmit plant-wide or school-wide time, or to add time to a video recorder, cable TV system, or industrial recorder. While the unit was intended to give you an 08:18:36 style time display of any reasonable size positioned anywhere you want on the TV, it can be made to display *any* combination of eight letters, numbers, punctuation, or blanks. For instance, you could display the calendar date, the TV channel number, the temperature, the weather "CLOUDY"; "WARMER"; "RAIN"; etc. Or you can use it as a security monitor, a calculator readout, or anywhere else you want to display a changing, limited amount of alphanumeric information on a TV set or oscilloscope. The unit gives you complete control of presence, size, position, and contrast.

The Revideo unit consists of 14 IC's on a 4½×6¾-inch PC board and needs 5 volts dc at 200 mA and -12 volts dc at 25 mA. This is picked up from the clock, a lab supply, or from a small custom supply. The cost of the IC's come to around \$23, buying from the back ads in *Radio-Electronics*, and a complete kit of all *other* parts is available, as are individual PC boards—see parts list.

The TV Revideo unit will interface with

the "1-2-4-8" counter outputs of any digital clock provided it uses the BCD code.

If you are using a one-chip or multiplexing clock circuit, you have to make sure a BCD output is available and then add suitable simple latches so that all the outputs (1, 2, 4, 8, 10, 20, 40 minutes, and 1, 2, 4, 8, 10, (20?) hours are available all at once in parallel form.

The final outputs must be TTL compatible. Regardless of what type of clock you use, you have to end up with these parallel BCD outputs. Since these rarely already exist as output terminals or pins, you usually add a *short* piece of multi-conductor flat cable to the respective pins on the counters in the clock.

Before you begin—note two important things: The TV set *must* be modified to bring out horizontal and vertical trigger pulses and a video input. If done properly, this is easy and cheap, and only adds to the value of the TV. In no way will it hurt normal operation. Secondly, if the receiver is a hot-chassis type, you'll have to either use an isolation transformer or else run the entire clock "hot-chassis" and properly safely-isolated as well. A schematic of the TV you're going to use is a must; a good scope will also be essential to modify the TV.

Understanding TV scanning

A TV set has a raster scan. Once every 1/60th of a second, a spot starts at the upper left hand corner and rapidly scans to the right and slowly downward, generating a series of 262 1/2 lines. Video is produced by controlling the brightness of, or *modulating*, the spot. During the next 1/60th of a second, the TV generates another 262 1/2 lines, putting these *between* the ones it did on the previous go-around. The two *interlaced* 1/60th second *fields* make up a 1/30th second *frame*, the time needed to display one com-

plete, stationary picture of 525 lines. By presenting 30 stationary frames per second, the pictures appear to move, since the eye cannot respond to each individual frame, but can only average them out for a final result. The fancy interlace scheme is used to reduce the apparent flicker.

The horizontal scan time, or the time to generate one line, is around 62 microseconds, of which 50 microseconds is spent in the actual scan and the rest in returning the *blanked* or turned off beam to the left side of the picture. A horizontal *synchronizing* pulse of some 5 microseconds is centered in the return blanking interval. It is used to lock the TV's horizontal scan to the scan at the TV camera. Obviously, the camera has to be looking at the same place the TV set is at the same time if we don't want a rolling or scrambled picture.

The vertical scan time lasts the entire 1/60th of a second. About 800 microseconds of this time is reserved for retrace. A vertical sync pulse 180 microseconds wide is centered in the blanking interval to lock the TV's vertical scan to that of the camera and the transmitter.

We can't change what the TV scan is doing or where it is at any particular time. This means we can't use stroke or segment style numerals on our time display. We have to use a bunch of dots, getting the dots to crop up at the right place and the right time to present a final numeral or character in a stationary and recognizable place.

We can easily sum an output signal from the Revideo unit right into the TV's video amplifier and present a composite time-on-picture display. The problem is to get the right dots in the right place at the right time. Fortunately, there is a stock MOS computer-on-a-chip that does most of the work for us.

To generate the dots, we have to derive a

horizontal trigger pulse and a vertical trigger pulse from the working TV and use these to synchronize and control the number generator. The vertical pulse is easily obtained from the vertical output stage and is attenuated to logic levels with external resistors and a coupling capacitor. While we could also use the horizontal output signal, this is usually a bit too strong and could detune the TV's flyback transformer. So, we have to find an equivalent positive-going horizontal pulse, such as off the plate or collector of the agc keyer. This signal is also attenuated with external resistors and capacitors to present a logic-level-sized, positive-going output pulse.

Fig. 1 is a block diagram of the TV Revideo unit, while Fig. 2 takes you through the timing sequence of a single field. The Revideo unit has two parts—the *timing* portion and the *signal processing* portion. The signal processing portion picks the right input number and converts it to the proper dot sequence at the proper place in the picture. The timing tells the signal processor when to do what, and locks things into the TV's vertical and horizontal scanning.

Choosing a character

We could get by with a numeral 3 dots wide by 5 dots high, but it wouldn't be very pretty, and there's no standard IC that will do the job. Instead, we use a computer standard 5-dot-high number or letter that we can get out of a standard ASCII alphanumeric character generator IC. To keep the timing simple and to still allow enough circuit setup time, we use three blank "udots" between each character. We also let the timing run for an eighth line at the bottom, generating all blank undots. This gets us by with a standard divide-by-eight counter.

While a seven-line-high character would do the job, it would be very small. It would also mean that you would have all sorts of interlace problems. So, we go to 14 lines of character height, putting identical information on both fields and solving both problems at once. Now, if you want the same thing to seven *pairs* of lines on *each* field, and end up with a 28-line-high character. Thus you have a choice of two possible character heights.

Now, we somehow have to get the right part of each numeral in the right place at the right time. This is what the Revideo unit is all about.

At the beginning of a field, a vertical trigger pulse trips a monostable delay that sets the vertical position of the numeral display. (Step 1, Fig. 2). Since the monostable could end up anywhere on the screen, it tells a *synchronizing* circuit to pick up the *next* eight *whole* horizontal lines and to allow a video output only during those lines. We use the first seven lines for numeric output; the final line is a blank. If, instead, we are using the double height characters, the *next* sixteen *whole* horizontal lines are picked, presenting 14 lines of numeral and 2 lines of blanks.

As we adjust the vertical position, the entire display moves up or down the screen to where we want it. Since the line counter is always working on *whole* horizontal lines, the vertical position control does not affect the side-to-side numeral positions, and the start of each numeral takes place on each field exactly the same distance from the side

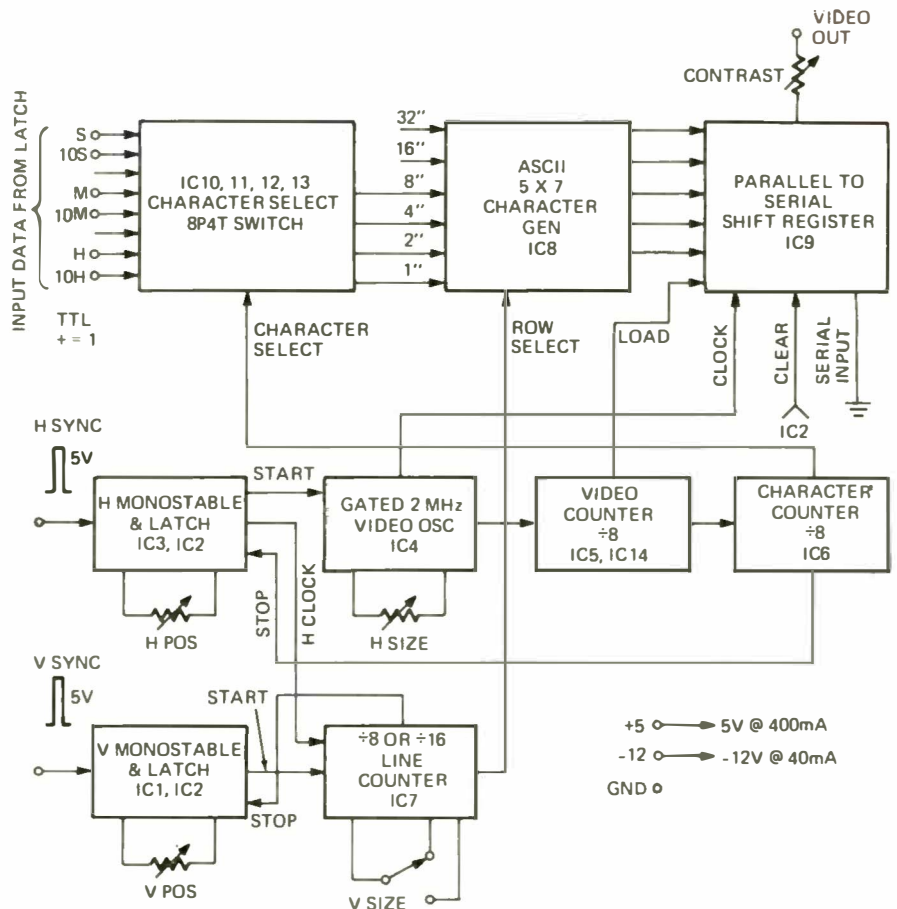


FIG. 1—REVIDEO UNIT for digital clocks, showing input and output connections.

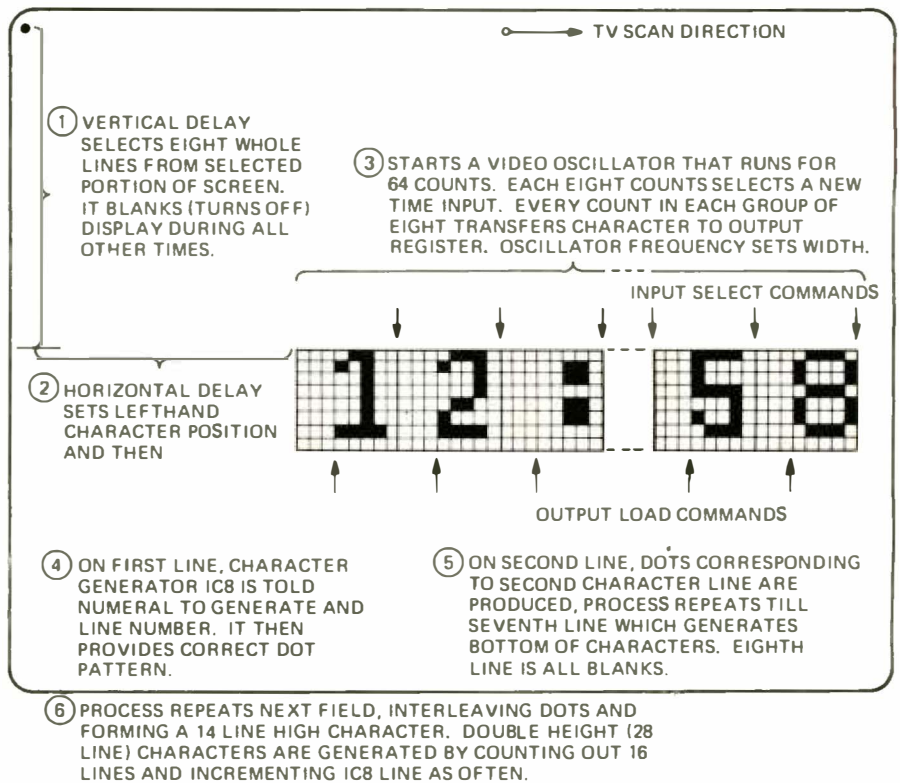


FIG. 2—TIMING OF A SINGLE FIELD

of the screen.

So much for the vertical action. Now (Step 2, Fig. 2) once each horizontal line, we start a delay monostable that tells us how far over to the right the display is going to be—this is our horizontal position control. After the delay is complete, a *video*

oscillator is started and counts out exactly 64 counts and then shuts down. The *frequency* of the video oscillator determines the spacing between counts, and thus determines the horizontal size of each numeral. The 64 counts are grouped into eight groups of eight counts each. The first group

is for the ten hours, the second for the hours, the third for a colon, and so on, out to the final eight, which are for the seconds information. The first three counts of each group is for the three blank-between-numeral undots and for settling time. The numeral undots and for settling time. The final five counts of each group are for the five possible numeral dots in each line.

The read-only memory computer character generator is the heart of the circuit. It has three input lines that tell it what line of the numeral it is working on, and six input lines that tell in which of 64 possible letters, numbers punctuation, or blanks to work on. When it is told which line of what character to generate, it outputs a group of five dots or undots that are needed for that part of that character. These five bits of information are then loaded into a shift register and marched out as video, nicely putting the right thing in the right place at the right time.

An eight-position selector switch precedes the character generator and picks the right input for each of the eight slots across the screen. The character generator combines this with an input from the line counter to decide what pattern of dots to produce. A three-count delay is allowed between the time we change the input to the character generator and load its output—this lets things settle down and gives the character generator a chance to operate. Thus, the output of the character generator is loaded into the shift register on the falling edge of the *third* count in each group of eight video oscillator pulses; the input selector is changed on the beginning of the *first* count in each group.

The character generator starts with the tops of all eight numerals on the first horizontal line. On the next line, its line counting input changes, and it puts the second row of dots down for each numeral. It continues this way down to the seventh line when it puts down the bottoms of all the numerals. The next line is a bunch of blanks, and after that, the circuit shuts down till the next field.

The ASCII character code


The input code for the character generator is shown in Fig. 3. The 64 possible inputs are represented by six lines. For numerals, the bottom four lines are simply the BCD or binary coded decimal representation of the numbers, exactly the same code used in the Superlock and the majority of digital clocks. If we wanted to have all the letters and numbers, we'd need a six-pole input selector. But for just numbers, we can hard-wire 1's (+5 volts) to the two most significant inputs, and we get by with only four poles worth of input selector. A colon is nicely a BCD "ten," or 1010.

If we brought all the leads out, there would be 32 of them on the input. It turns out we can save on input wires by hardwiring what we aren't going to change or don't need. For instance, we can put the colons in permanently in positions three and six. We don't need the 80 hours and 40 hours inputs, so we can make these permanently zero or ground. We don't need the 20 hours input if we are using only a 12-hour display, but we do need it for the 24-hour version. Similarly, we don't need the 80 minutes and 80 seconds inputs; these can also be zeros. This reduces the input leads to 19 or 20. These can be a small flat cable (or two) a foot long

ASCII CHARACTER CODE			
fedcba		fedcba	
000000	@	100000	BLANK
000001	A	100001	!
000010	B	100010	"
000011	C	100011	#
000100	D	100100	\$
000101	E	100101	%
000110	F	100110	&
000111	G	100111	'
001000	H	101000	(
001001	I	101001)
001010	J	101010	*
001011	K	101011	+
001100	L	101100	COMMA
001101	M	101101	DASH
001110	N	101110	PERIOD
001111	O	101111	/
010000	P	110000	0
010001	Q	110001	1
010010	R	110010	2
010011	S	110011	3
010100	T	110100	4
010101	U	110101	5
010110	V	110110	6
010111	W	110111	7
011000	X	111000	8
011001	Y	111001	9
011010	Z	111010	:
011011		111011	;
011100	\	111100	<
011101		111101	=
011110	^	111110	>
011111	UNDERLINE	111111	?

a = a₀ = WEIGHT "1" = PIN 17 OF ICB (FIG. 1)
 b = a₁ = WEIGHT "2" = PIN 18 OF ICB
 c = a₂ = WEIGHT "4" = PIN 19 OF ICB
 d = a₃ = WEIGHT "8" = PIN 20 OF ICB
 e = a₄ = WEIGHT "16" = PIN 21 OF ICB
 f = a₅ = WEIGHT "32" = PIN 22 OF ICB
 "1" = +3 TO +5 VOLTS
 "0" = GROUND

FIG. 3—ASCII CODE (The American Standard Code for information Interchange).

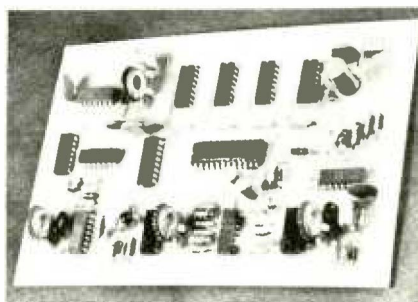

THE REVIDEO UNIT, carefully constructed, works as well as it looks.

that plugs directly into the readout sockets on the Superlock.

The circuit

With these operating principles in mind, let's turn to the actual circuit and parts lists of Figs. 4 and 5. The H and V inputs are conditioned with Q1-D4 and Q2-D5 respectively and then fed to monostables IC3 and IC1 for the horizontal and vertical position delays. At the end of their delay times, the pair of latches in IC2 are respectively set. The vertical latch (pins 8-12) releases the clear on a divide-by-eight or a divide-by-sixteen counter IC7 that counts out the horizontal lines used for the active portion of the display. The V SIZE control jumper

lets you pick a normal or double height character.

Once each horizontal line, the horizontal latch (pins 1 to 16 on IC2) releases a clearing clamp on the video oscillator IC4, the divide-by-eight video counter (IC5) and the cascaded divide-by-eight character counter (IC6). The video oscillator is a free running astable multivibrator when it is not being clamped by IC2. Its frequency is coarsely controlled by C11 and finely adjusted by R24, the horizontal size control. After exactly 64 counts, the H latch is cleared, the counters are clamped to 0000 and the video oscillator is stopped to await the next horizontal line.

The video counter goes around eight times and controls the output loading and spacing. It changes the input selector address just before its *first* count, and provides a shift register IC9 (Fig. 5) load count on the falling edge of its *third* count. This automatically transfers the contents of the character generator IC8 to the output register after a three-count settling delay. Three undots, or the space between numerals is generated during the three-count settling time. The final five counts of each numeral sequence are for the actual numeral video.

The character counter goes around only once per line, stepping a four-pole, eight-position input data selector IC10-13 once around as needed, routing the report inputs to the character generator in the right time slots. Character generator IC8 receives this data, along with a what-line-is-it? command from the line counter IC7. The character generator then outputs the proper dot combination to the output register IC9 which in turn marches the dots out as video.

Building it

PC boards are commercially available for this project, as are parts kits—see the parts list. If you are building and etching your own board instead, a full size replica appears in Fig. 6. Components are located as shown in Fig. 7.

Start assembly with the jumpers and the smaller components, followed up by the IC's and finally the control pots. Use a small iron and fine solder and be sure to observe which IC goes where and the code notch and dot on each one. Also, watch out for diode and electrolytic capacitor polarities. Chances are you'll want to start with the larger character size, so jumpers the two upper "28" holes in the V SIZE box. Do not unwrap IC8 or remove it from its protective foam until you have modified the TV suitable and have *completely* tested the rest of your circuit.

Modifying your television

You'll need three modifications on your TV. One is to provide a new video input to sum the time on top of the existing program. One is to derive a narrow, positive-going, vertical sync pulse of 3 to 5 volts amplitude across a 10,000-ohm resistor. Finally, you have to derive a suitable narrow positive horizontal sync pulse of 3-5 volts across a 10,000-ohm resistor. *Any* method you use that doesn't obviously affect the TV operation and still gets the job done is acceptable, and the best way varies from brand to brand and model to model.

Before you modify your television, sit down carefully with a complete schematic or *PhotoFact* set and locate suitable tie-in

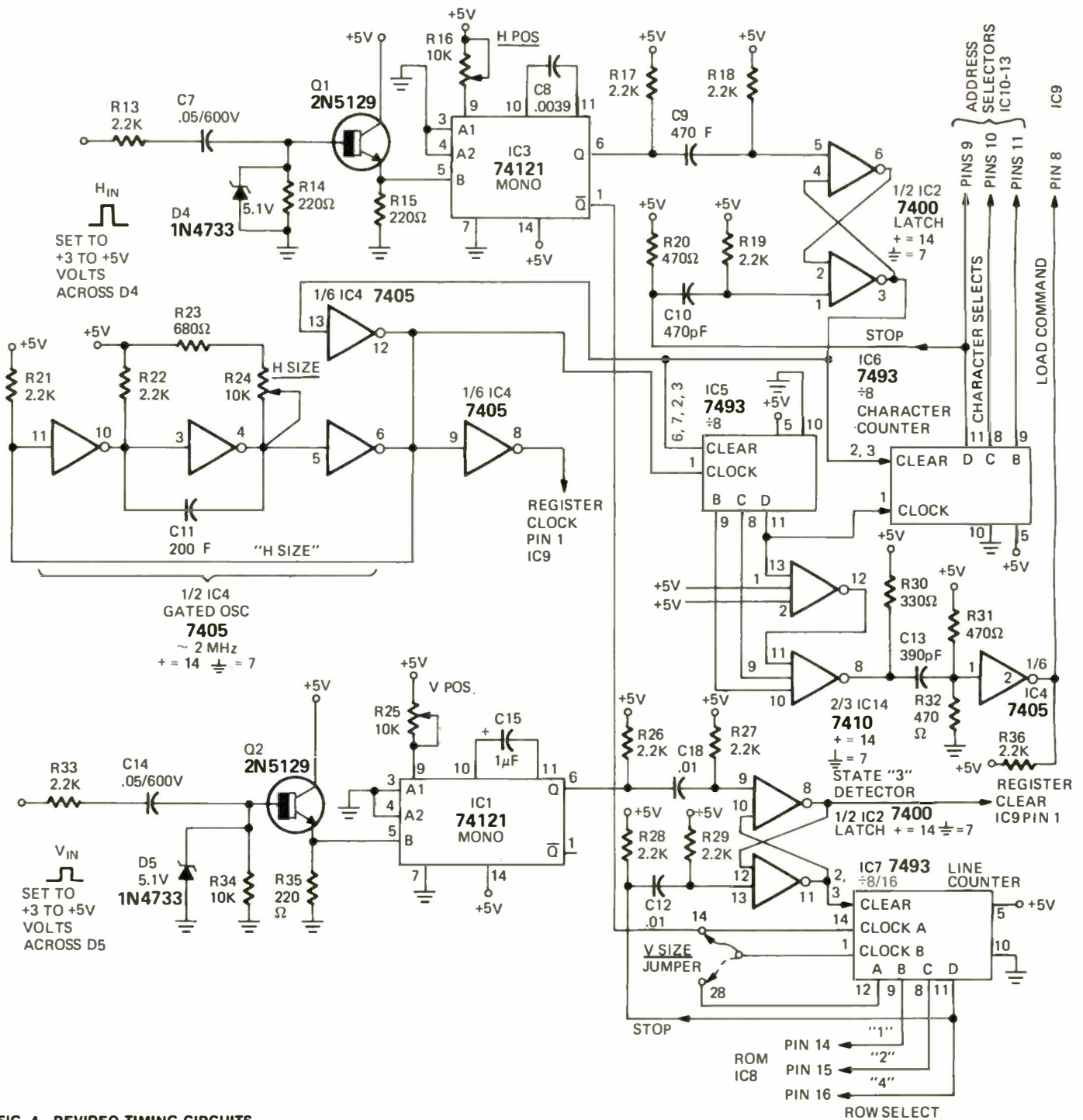


FIG. 4—REVIDEO TIMING CIRCUITS.

points. An oscilloscope is almost essential for this, even if you have extensive electronics experience. Fig. 8 suggests some possible interface points.


Let's start with the video. This can usually be injected into the grid or base of the first video amplifier stage, most likely through a 3,300-ohm series resistor and 0.1- μ F coupling capacitor. The optimum network here is one that doesn't degrade the normal picture response, yet at the same time provides enough numeral contrast. Be sure to pick a point that gives you *white* numerals. This means a point in the circuit where more positive means *whiter*. Adjust the value of R12 for the desired numeral contrast.

On a tube TV, a whole bunch of attenuation will be required to bring the trigger signals down to size. One good place to et the vertical trigger signal is the plate or col-

COMPLETE

- C1, C2—10- μ F, 15-volt electrolytic
- C3—30- μ F, 6-volt electrolytic
- C4, C5, C16, C17, C18—0.1- μ F, 10-volt disc ceramic
- C6, C7, C14—0.05- μ F, 600-volt mylar
- C8—.0039- μ F polystyrene
- C9, C10—470-pF poly, mica, or disc
- C11—200-pF polystyrene or mica
- C12, C16—0.01- μ F, 10-volt disc ceramic
- C13—390-pF polystyrene or mica
- C15—1- μ F, 15-volt tantalum electrolytic
- D1—1N4001 or equivalent silicon power diode
- D2, D3, D4, D5—5.1-volt, 1-watt Zener diode, 1N4733 or equivalent
- IC1, IC3—72121 TTL monostable
- IC2—7400 TTL quad two-input gate
- IC4—7405 TTL open collector hex inverter

- IC5, IC6, IC7—7493 TTL divide by sixteen
- IC8—2513 ASCII character generator (Signetics)
- IC9—7496 TTL five-bit shift register
- IC10 to IC 13—74151 TTL one-of-eight selector
- IC14—7410 TTL triple three-input gate
- Q1, Q2—2N5129 transistor
- R1—27-ohm, carbon
- R2—150-ohm $\frac{1}{2}$ -watt carbon
- R3, R6, R9, R13, R17, R22, R, R26, R29, R33, R36—2.2K, carbon
- R7—1K upright mounting PC potentiometer
- R8—1K, carbon
- R14, R34—10K, carbon
- R16, R24, R25—10K upright mounting PC potentiometer
- R23—680-ohm carbon

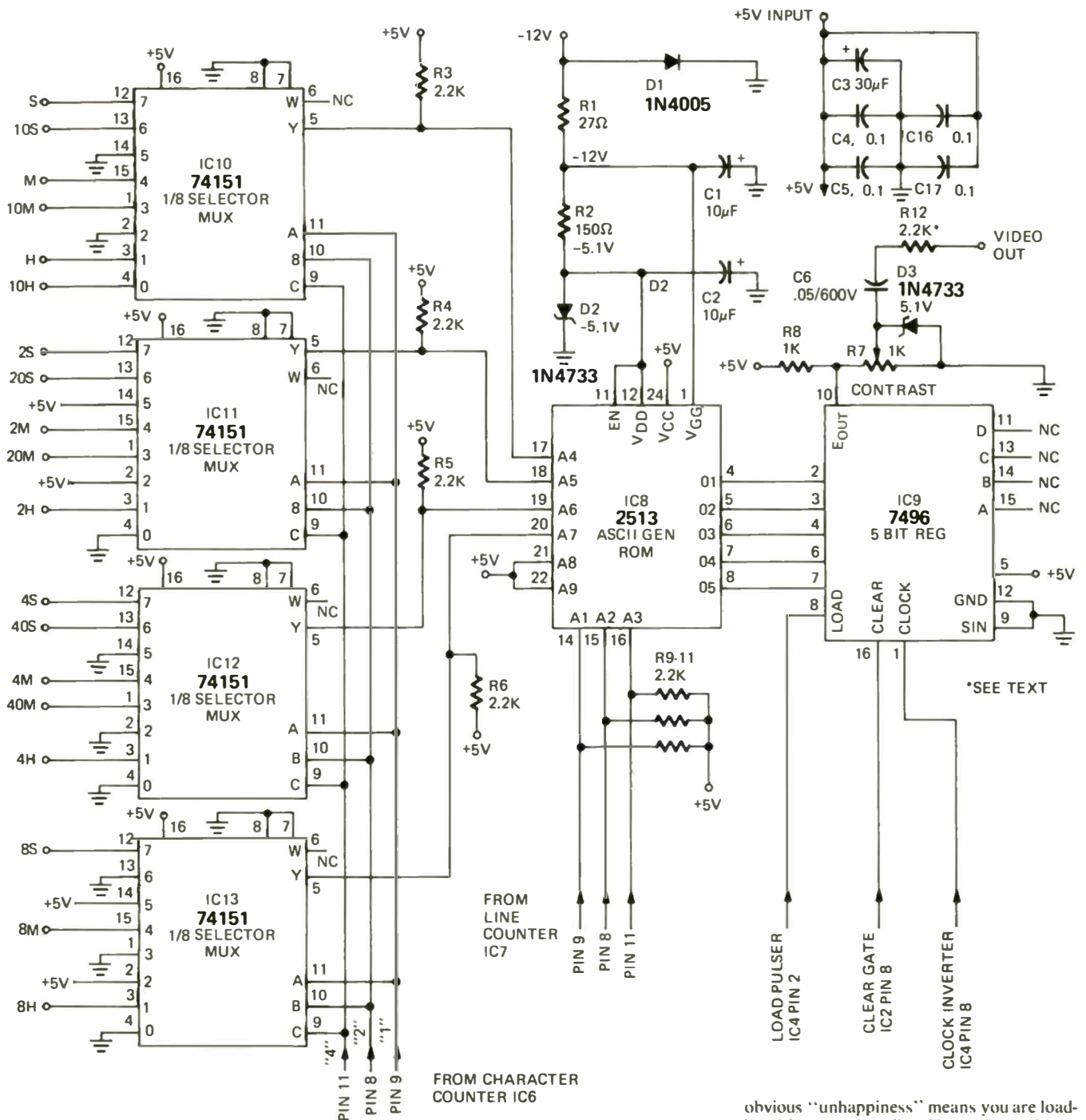

PARTS LIST

R29—4.7K, carbon
 R30—330-ohm, carbon
 R20, R26, R31, R32—470-ohm, carbon
 R15, R35—220-ohm, carbon

All resistors 1/4-watt unless noted

Miscellaneous

PC Board, 4 × 6 1/2 inches; PC terminals, optional (25); No. 24 wire jumpers and sleeving; mounting hardware; Flat 16-conductor input cable (2 lengths); solder; TV interface connector and lead kit (optional); gating switch (optional);

NOTE: The following is available from Southwest Technical Products, 219 West Rhapsody, San Antonio, Texas,

78216; Circuit Board, etched and drilled No. RV-1, \$2.85

(IC's are considerably cheaper from surplus and volume suppliers listed in **Radio-Electronics** ads than could be offered as part of a kit—the kit is thus split to give the **Radio-Electronics** reader the lowest possible unit price.)

lector of the vertical output stage. This will be several hundred volts high and a suitable narrow, positive going spike. Cut it down to size with two series 470K, 1-watt resistors and a 005-μF, 600-volt coupling capacitor. Use two series capacitors if the voltage is higher. When the network is added to the TV, nothing drastic should happen. A slight change in picture height or hold setting might occur, but any tearing, breakup, or

obvious "unhappiness" means you are loading things too heavily. The attenuated output has to drive a TTL monostable. It should stay below 0.8 volts most of the time; the narrow positive portion of the output should be 3 to 5 volts high with the Reviduo unit connected. Unconnected, the signal should be *twice* as great (6-10 volts).

Don't try using the horizontal output stage as a trigger point—besides being lethal we could detune the flyback and cause all sorts of problems. So, look around for another, tamer narrow horizontal trigger pulse. On older tube TV's the plate of the agc keyer should have a several-hundred-volt narrow positive pulse suitable for our needs. Attenuate it down to the same size as the vertical trigger is—mostly below 0.8 volts except for a narrow, 3 to 5-volt positive pulse with the Reviduo unit connected, 6-10 volts on open circuit.

Which transistor TV's, the voltages generally will be lower and somewhat less attenuation (lower value resistors) will be

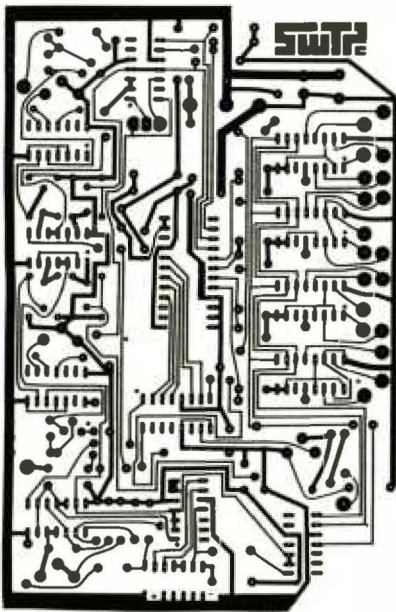


FIG. 6—LAYOUT OF THE PRINTED CIRCUIT BOARD, one-half actual size.

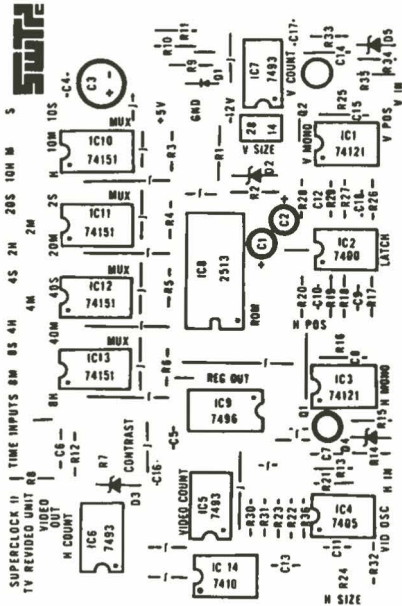


FIG. 7—THE COMPONENTS LAYOUT.

needed. Since the total energy you need for triggering is negligible compared to the normal circuit needs of the TV, you should have no problem after a try or two. Above all, work with the schematic and the scope when you're modifying the TV and don't connect the Revideo unit up until you are *sure* you have safe and reasonable trigger signals. Remember that connecting the Revideo unit will cut the trigger amplitude in half—from 6-10 volts to between 3 and 5 volts.

Preliminary checkout

You'll also need a ground lead between the TV and the Revideo unit. A complete set of system interconnections is shown in Fig. 8. Remember that if the TV has a hot chassis you'll have to use an isolation transformer or live with a completely "hands off" system!

Leave IC8 uninstalled and the clock unconnected for the initial checkout. Apply suitable supply power and complete the television set to Revideo unit connections.

SAFETY WARNING: IF TV IS HOT CHASSIS, USE ISOLATION TRANSFORMER OR COMPLETELY INSULATE ENTIRE CIRCUIT!

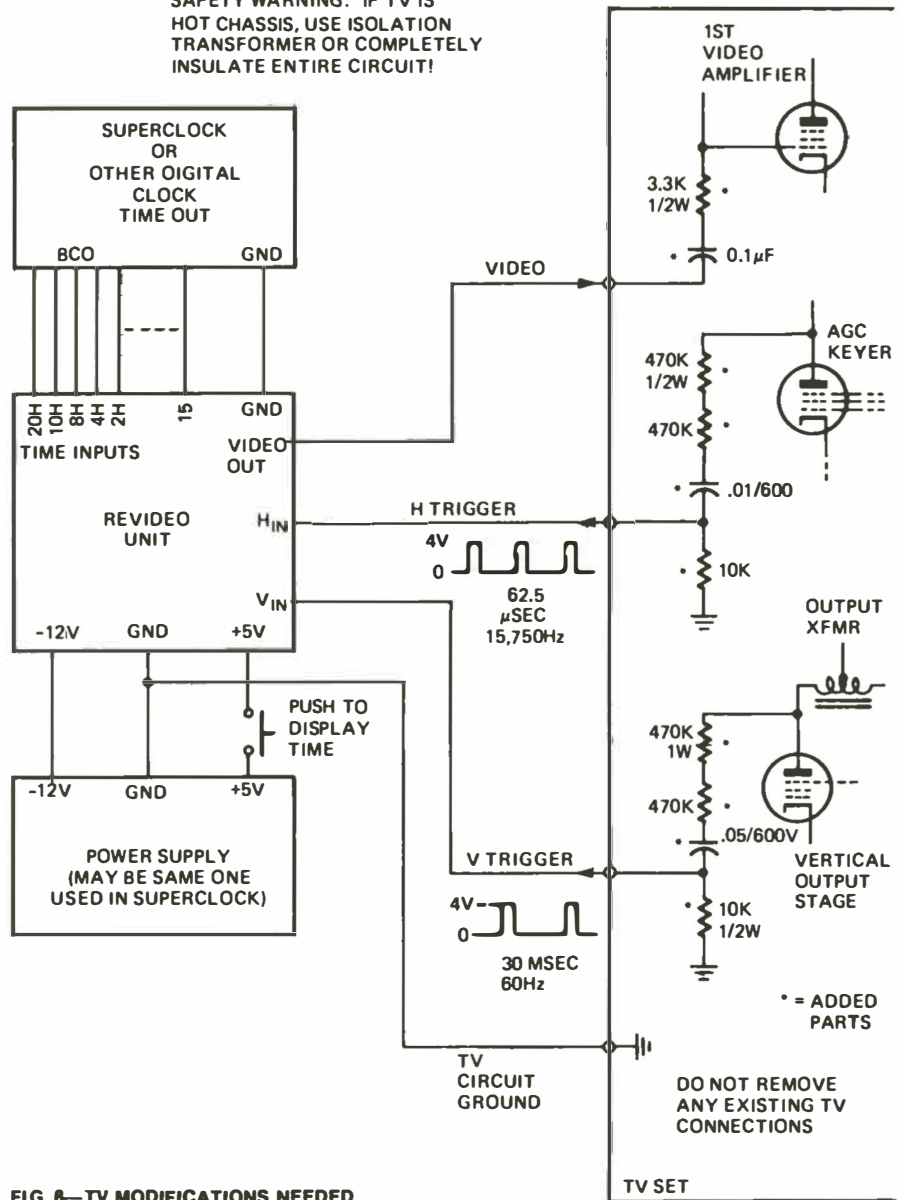


FIG. 8—TV MODIFICATIONS NEEDED.

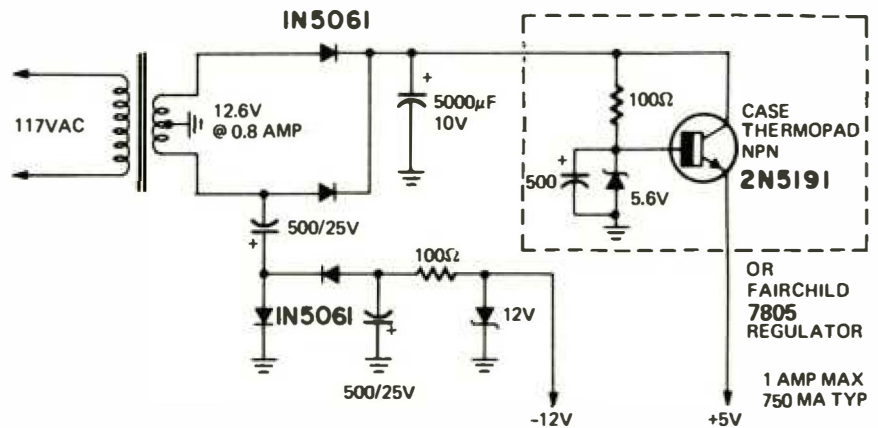


FIG. 9—OPTIONAL POWER SUPPLY

(An optional power supply is shown in Fig 9; use it only if you can't get power from the clock, the TV or a handy bench supply.)

If everything is working right, you should have eight white boxes where the numerals are to go, and you can move them around and change their size as you want to.

If you don't have the boxes, use a scope

to debug. Check first for proper trigger pulses on IC1 and IC3, followed by proper operation of the video oscillator and the three counters, finishing up with the output register and the stage-three decoder IC14. Usually trouble is caused by the input networks being wrong or crossed to the wrong inputs.

(continued on page 94)

ELECTRONIC TECHNICIANS!

Raise your professional standing
and prepare for promotion! Win
your diploma in

ENGINEERING MATHEMATICS

from the Indiana Home
Study Institute

We are proud to announce two great
new courses in Engineering Mathematics
for the electronic industry.

These unusual courses are the result of
many years of study and thought by the
President of Indiana Home Study, who
has personally lectured in the classroom
to thousands of men, from all walks of
life, on mathematics, and electrical and
electronic engineering.

You will have to see the lessons to ap-
preciate them!

NOW you can master engineering
mathematics and actually enjoy doing it!

WE ARE THIS SURE: you sign no
contracts—you order your lessons on a
money-back guarantee.

In plain language, if you aren't satis-
fied you don't pay, and there are no
strings attached.

Write today for more information and
your outline of courses.

You have nothing to lose, and every-
thing to gain!

The INDIANA HOME STUDY INSTITUTE


Dept. RE-974, P.O. Box 1189, Panama City, Fla.
32401

Circle 76 on reader service card

FREE ALARM SYSTEM CATALOG



Controls

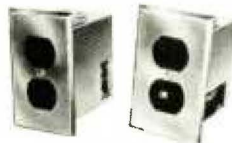

Detectors



Sirens

Full line of professional burglar
and fire alarm systems and sup-
plies. 96 pages, 450 items. Off-the-
shelf delivery.



mountain west alarm
4215 n. 16th st.
phoenix, az. 85016
(602) 263-8831

Circle 77 on reader service card

MEASURE HI-FI PERFORMANCE (continued from page 63)

Additional measurements

Another convenient pushbutton on
the analyzer permits the user to di-
rectly measure and read the wattage
consumed by any audio product from
the power line source. There is also an
external input to the digital readout
module which lets you read the amp-
litude of any sinusoidal waveform up to
250 volts rms.

External inputs are provided through
which signals may be fed into the in-
strument in the event that audio fre-
quencies other than those built in are
required for any reason. Such signals
will, of course, have their amplitudes
read directly by the digital module and
are fully controllable by the switches
and multiturn attenuation potentiomet-
ers of the analyzer.

The acquisition of the McAdam
audio analyzer has, of course, sim-
plified many of the audio measure-
ments which I am called upon to make
almost daily and I have found that it
is relatively easy to interface this equip-
ment with the rf equipment which is
used for AM and FM measurements.
For example, the Sound Technology
FM generator model 1000A, shown
standing atop my now displaced audio
generator in Fig. 1, has provisions for
external modulation. By modulating it
with the available audio tones from the
McAdam analyzer and connecting
tuner or receiver under test to the out-
put terminals of the analyzer, full use
can be made of the distortion meas-
urement facilities of the analyzer and
THD as well as S/N readings can be
made digitally as well. By continuing to
use the internally supplied stereo com-
posite signal generating facilities of the
FM generator, separation measure-
ments can also easily be made using the
generator in combination with the
McAdam analyzer.

The McAdam analyzer is not inex-
pensive, retailing for \$3450.00, but
even in the short time we have had an
opportunity to use it in our daily lab
work it has begun to pay off in terms of
time saved and increased accuracy and
reliability of measured results. R-E

Life Share!

Share your life with a
high school student from
another culture.

American Field Service
International Scholarships
313 E. 43rd St., N.Y., N.Y. 10017

TIME ON TV SCREEN

(continued from page 42)

Once you have the eight white boxes,
carefully measure the voltages where IC8 is
to go—+5 on pin 24; -5 on 11 and 12; and
finally -12 on pin 1. Reverse supply voltage
will instantly ruin IC13, so even with the
idiot-proofing network D1, R1 be careful!

IC8 is a MOS integrated circuit, and ex-
ceptionally careless handling could damage
it. Leave it in the case and protective foam
till you are ready to use it, then quickly sol-
der it in place with a small soldering iron,
watching to get the code dot and notch cor-
rect. After it is soldered in place, the circuit
will protect the IC from most damage.

Reapply supply power, and the eight
boxes should now read 1:?:?:?? if you have
a 12-hour system and 3?:?:?? if you have a
2400-hour one. The unconnected inputs are
"read" as digital "1"s, as are +5 signals.
Only a ground is read as "0". Do not con-
nect anything to your clock until you have
the exact display called for above. Once you
are certain all is well, connect up the mul-
ticonductor cable to the proper place in your
Superclock (either the inputs to the readouts
or the 1-2-4-8 outputs of the various coun-
ters). Keep these short, preferably under 15
inches. The TV interconnects can be
reasonably long, but avoid running across
the room with them. When the clock is con-
nected, you should have the correct time to
your TV set and the project is complete.

Using it

Remember, you can turn the time display
off and on by applying or removing the +5,
by breaking the video line, or by breaking
the vertical trigger line. If you experience
some character breakup at the minimum
horizontal width settings of the display, you
can increase the -12V supply by a volt to
-13, or, if you're real brave, you can short
out R1. Should you want a bigger than the
largest available time display, increase C11.
For a very small display, decrease C11 and
you can go down to the breakup point. With
the circuit we've shown you, the minimum
display size will be slightly wider than
shown in the lead photo. You should be able
to use the available controls to move the
display most anywhere you want to place it
on the screen and almost any size, within
reasonable limits.

If you want to display something besides
the time, you can rework the input data
selectors and perhaps add two more to pick
up the total alphanumeric capability of this
circuit.

Should you want lots more than 8 nume-
rals at a time and want internal storage as
well, a much more elaborate TV
ALPHABETIZER system is in the works here
at RADIO-ELECTRONICS. We'll be telling you
about it shortly. In the meantime, good luck
on this project. R-E