

**BUILD DIRECT  
LOW-COST DIGITAL  
LOGIC IC'S  
ALLOW EASY CONSTRUCTION  
OF 5-RANGE METER  
COVERING THE SPECTRUM  
FROM 5 HZ TO 1.0 MHZ**

By **DON LANCASTER**



**E**VER DREAM of owning a good frequency counter? The \$500-and-up instruments are tops for all sorts of experimental and industrial work, but the accurate clock and complex decoding circuitry they use puts them well out of reach of most experimenters. But how about a frequency meter? About \$12 worth of semiconductors, integrated circuits, and other parts can put you in

command of a five-range, linear scale meter, good from 5 Hz to 1 MHz. It has an input sensitivity of 30 millivolts r.m.s., accepts any waveshape with no loss of accuracy, and automatically calibrates itself simply by borrowing the 60-Hz reference belonging to the local power company. The integrated circuits and a printed board make it a snap to put together.

This frequency meter is perfect for checking the performance of experimental audio oscillators, tone generators, and square-wave signal sources, and is particularly handy if you're working with RTTY, FM multiplex decoders, tone-signaling circuits, or electronic musical instruments. It's a "must have" instrument for working with transistor or SCR power inverters when it comes time to set—and keep—the operating frequency right on 60 Hz, and it's useful for checking out the performance of engine-driven emergency power units.

Add an external oscillator, and the unit becomes an accurate LC bridge for determining the value of an inductance or capacitance. And, finally, you can make the meter count anything you can convert into repetitive electrical pulses by adding a small generator and a photoelectric pickup, or something similar;

then the meter is an accurate, wide-range linear-scale tachometer.

**How It Works.** The input signals are amplified and inverted by transistor *Q1*, as shown in Fig. 1. This transistor drives a Schmitt trigger circuit (*IC1*) whose output snaps from ground to +3.9 volts the instant the input signal goes positive above a certain threshold level. The rise time of *IC1*'s output (from pin 6) is independent of the shape of the input signal, so a rectangular waveform of identical frequency to the input results.

Capacitor *C8* and resistor *R13* differentiate the square wave to produce a positive trigger pulse every time *IC1* snaps on. These pulses trigger *IC2* (a monostable multivibrator), which also snaps on, and stays on for a precise time interval determined by *R8*, *R15*, and a selected range capacitor (from *C9*

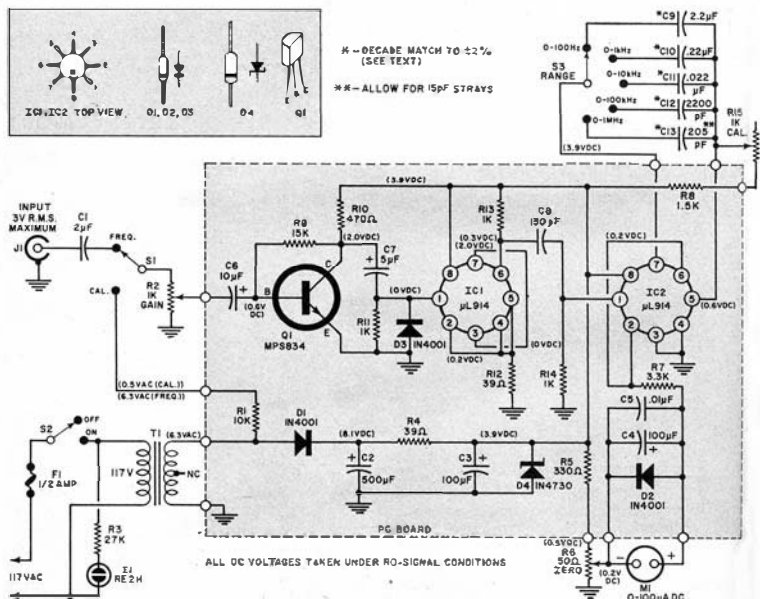


Fig. 1. Although only one transistor is shown, the two IC's contain five transistors and nine resistors. The circuit is self-checking from commercial power line through S1 (calibrate position) and resistor R1.

## PARTS LIST\*

- C1—3- $\mu$ F, 200-volt paper or Mylar capacitor (NOT an electrolytic)  
 C2—500- $\mu$ F, 25-volt electrolytic capacitor  
 C3—100- $\mu$ F, 15-volt electrolytic capacitor  
 C4—100- $\mu$ F, 6-volt electrolytic capacitor  
 C5—0.01- $\mu$ F, 50-volt Mylar or paper capacitor  
 C6—10- $\mu$ F, 10-volt electrolytic capacitor  
 C7—5- $\mu$ F, 10-volt electrolytic capacitor  
 C8—150- $\mu$ F mica or disc ceramic capacitor  
 C9—2.2- $\mu$ F, 50-volt Mylar or paper capacitor (NOT an electrolytic)  
 C10—0.22- $\mu$ F, 50-volt Mylar or paper capacitor  
 C11—0.022- $\mu$ F, 50-volt Mylar or paper capacitor  
 C12—2200- $\mu$ F Mylar, paper, mica, or disc ceramic capacitor  
 C13—205- $\mu$ F mica or disc ceramic capacitor (allows for 15  $\mu$ F of stray and circuit capacitance)  
 D1, D2, D3—Silicon diode, 200 mA, 50 PIV (1N4001 or similar)\*\*  
 D4—Zener diode, 3.9 volts, 1 watt (1N4730A or similar)\*\*  
 F1— $\frac{1}{2}$ -ampere fuse (and fuse holder)  
 I1—Neo lamp  
 IC1, IC2— $\mu$ L919 CMOS integrated circuit (Fairchild)\*\*  
 J1—Phono jack  
 M1—0-100 d.c. micrometer,  $\frac{1}{16}$ " rectangular (Knight S2 A 7206, or similar)  
 Q1—Silicon transistor (Motorola MFS2923 or MPS834)\*\*  
 R1—10,000-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 R2, R15—1000-ohm, linear-taper carbon potentiometer  
 R3—27,000-ohm,  $\frac{1}{2}$ -watt resistor (may be a part of I1)  
 R4—39-ohm, 1-watt carbon resistor  
 R5—510-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 R6—30-ohm, linear-taper carbon potentiometer  
 R7—3300-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 R8—1300-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 R9—15,000-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 R10—470-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 R11, R12, R14—1000-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 R13—59-ohm,  $\frac{1}{4}$ -watt carbon resistor  
 S1—S.p.d. slide switch (Wet G323, or similar)  
 S2—S.p.d. slide switch (Wet G324, or similar)  
 S3—Single-pole, five-position, non-throwing selector switch (Mallory 31151, or similar)  
 T1—Filament transformer, 6.3 volts, 0.6 ampere (Knight S4 A 1416, Stancor P6465, Thoradson 21F21, or similar)  
 1— $\frac{1}{8}$ " x  $2\frac{3}{4}$ " x  $5\frac{1}{2}$ " single-sided copper printed circuit board\*\*\*  
 1— $3\frac{1}{2}$ " x 6" x 3" aluminum box (Bnd C.U.2109A, or similar)  
 Misc.—Linc cord and strain relief, handgrip knobs (4), rubber feet (4), PC terminals (11), mounting hardware for M1 and I1, wire, solder, etc.

\* Accuracy of instrument depends directly upon accuracy with which C10 through C13 are exact decade submultiples of C9.

\*\* A kit of all semiconductors is available from Hamilton Electro of Arizona, 1741 N. 28 St., Phoenix, Ariz. 85009, for \$4.50, postpaid in USA. Stock #ZX-53.

\*\*\* The printed board is  $\frac{1}{16}$ " etched and drilled G-10 fiberglass is available for \$2.50 from Southwest Technical Products Corp., 219 W. Rhapsody, San Antonio, Texas 78216. Most of the other parts as well as complete kits are also available—write to Southwest Technical for complete list and prices.

through C13). Each capacitor provides a time delay ten times that of its neighbor, resulting in five decade frequency ranges. Calibrate control R15 sets the time delay to a value that causes a 60-Hz input signal to read exactly 60 on the 100-Hz range.

How often IC2 snaps on is determined by the input frequency, while how long it stays on is determined by the range switch-selected capacitor. The ratio of on time to off time linearly increases with increasing frequency. Resistor R7 charges up C4 and C5 (an integrator) to a voltage whose average value equals the ratio of on to off time. Meter M1 then indicates this average voltage as frequency.

Zero control R6 provides a small d.c. voltage to buck out the saturation effect of IC2, while D2 protects the meter from overload if an input frequency higher than full scale is encountered. A conventional zener-regulated +3.9-volt d.c. supply is used. Switch S1 and resistor R1 route the 60-Hz power to the input for calibration.

The 100-Hz scale accuracy depends solely upon how closely you can read the meter, while the scale-to-scale accuracy depends upon how closely the range capacitors (C9 through C13) are exact decade multiples. An accuracy of better than  $\pm 3\%$  should be easily obtained with a quality meter and careful capacitor selection.

**Construction.** The two IC's together replace five transistors and nine resistors, which, if bought separately, would cost eight dollars, or well over twice that of the IC's, not counting the extra assembly time and trouble.

Buy (see Parts List), or etch, cut, and drill the printed circuit board and mount the components as shown in Figs. 2, 3, and 5. Watch the polarity on all semiconductors and electrolytic capacitors. On IC1 and IC2, make certain lead 8 (center lead of flat side, having a red dot) goes to the +3.9-volt supply.

Mount the meter, pilot lamp, Range switch S3, Gain control R2, input jack J1, Zero control R6, on/off switch S2, calibration switch S1, and calibration potentiometer R15 on a suitable front panel as shown in the photo on page 53. Mount the PC board and the remainder of the components within the selected

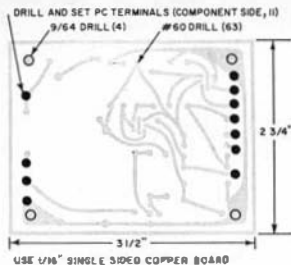


Fig. 2 (above). Drilling details for the printed board. Actual-size board is shown on page 98.


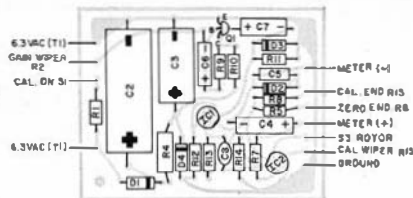


Fig. 3. (above, right). Component location on board, and connections to remainder of circuit.

Fig. 4 (right). Interior of the frequency meter showing general location of parts other than those already mounted on this printed board.

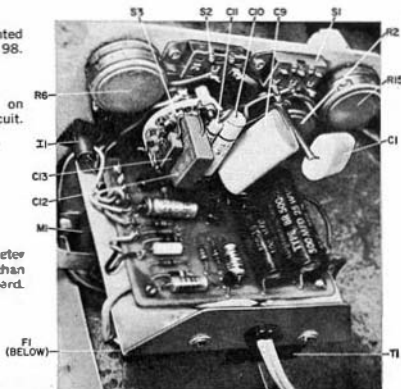

metal enclosure. Use Fig. 3 as a guide for interconnecting the PC board with the remainder of the system.

The accuracy of the instrument on the four upper scales depends entirely upon how closely range capacitors  $C1\theta$  through  $C13$  are exact decade submultiples of  $C9$ . One source of matched capacitors is given in the Parts List. Otherwise, by using an LC bridge, a quality oscilloscope, or a good audio oscillator, you can trim the capacitance (and therefore, the on time of  $IC2$ ) so that the frequency indication on  $M1$  has exact scale-to-scale calibration.

When the capacitors are accurate, you'll have a correct frequency reading on *any* scale without having to retouch the *Calibrate* control, and with a power-line calibration, you can rest assured that all scales will be accurate.

**Operating Hints.** Always turn the gain control fully counterclockwise before you make any measurement or connect the instrument to a live circuit, or you might risk damage to  $Q1$ . Calibrate the instrument each time you use it by zeroing the meter (with front-panel Zero control  $R6$ ), selecting the 100-Hz range, and setting the *Freq/60 Hz* switch ( $S1$ ) to 60 Hz. Bring the Gain control up a quarter turn and adjust the meter to a steady "60" reading using the *Calibrate* potentiometer. Set the *Freq/60 Hz* switch to *Freq*, and you're all set to measure.

Keep the input amplitude under 3 volts r.m.s. maximum. If you're working with higher signal levels, add a resistive divider to cut the level down. You may safely connect the input to any d.c. level within the breakdown rating of  $C1$ .

(Continued on page 98)

# NEW Mosley CB Stack 'It Beam

Extra gain for nearly 1/2 the previous cost of stacking Mosley beams.

4610 N. Lindbergh Blvd.  
Mosley Electronics Inc. Bridgeton Missouri 63042

Please send me FREE of charge and obligation, literature on the STACK 'IT beams.

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_

Zip Code No. \_\_\_\_\_

**Mosley Electronics Inc.** #108

4610 N. Lindbergh Blvd. Bridgeton Mo. 63042

CIRCLE NO. 26 ON READER SERVICE PAGE



SMALL BUT POWERFUL

DON'T BE FOOLED BY  
IMITATIONS!  
Get the ORIGINAL

SYDMUR SOLID STATE "CO" IGNITION SYSTEM!

High Quality Components used throughout. Fiberglass Printed Circuit Board. Unitized Construction. Simplified Kit Assembly.

Construction Article in Nov. 1966 Popular Electronics  
Thousands of satisfied customers.

Write for Free Literature TODAY.

COMPAC Assembled . . . \$34.75\*

COMPAC KIT . . . . . 24.95\*

\*Add 75c for mailing and handling

N.Y. State Residents add Sales Tax.

SYDMUR ELECTRONICS SPECIALTIES  
1268 E. 12th St. Brooklyn, N.Y. 11230

WRITE  
NOW FOR  
1968  
SENT FREE

## McGEE'S CATALOG

1001 BARGAINS IN

SPEAKERS—PARTS—TUBES—HIGH FIDELITY  
COMPONENTS—RECORD CHANGERS—

Turn Receivers—Kits—Everything in Electronics

1901 McGee Street, Kansas City, (PE), Missouri 64108

## IC FREQ METER

(Continued from page 56)

Avoid pegging the meter by always starting one range *above* the frequency you want to measure. Best operation occurs when the *Gain* control is advanced 3/4th of a turn beyond the point where the meter first produces a steady indication.

For power inverter work, there's a different way to use the frequency meter. Calibrate the instrument against the 60-Hz power line and then plug the frequency meter's power line cord into the in-



Fig. 5. Actual size layout of PC board. Drill as shown in Fig. 2; mount components as per Fig. 3.

verter, leaving the *Freq/60 Hz* switch in the 60 Hz position. Now, read the frequency directly. The zener-regulated supply automatically takes care of any inverter voltage from 70 to 160 volts, at any frequency from 30 to 1200 Hz.

In cases where you're measuring pulses or other low duty cycle signals, you'll get best results with a narrow, *negative-going* input waveform. -30-