



BUILD A MUSICAL **PITCH REFERENCE**

INTEGRATED CIRCUITS ARE USED TO DEVELOP
TWELVE MIDDLE TONES FOR ORGAN TUNEUP

BY DON LANCASTER

NOTHING MARS THE PLEASURE of playing a musical instrument like having it be out of tune. If your ear is good, you can tune a guitar or a violin using a pitch pipe or a tuning fork. Tuning a piano or an organ is more difficult, requiring complex equipment, lots of experience, and an expert ear.

Tuning a musical instrument of any type is made almost foolproof if you

have available a source of musical pitches covering one whole octave. That's what the "Pitch Reference" does. It is an integrated-circuit frequency synthesizer that generates twelve of the middle notes of the equally tempered musical scale to an accuracy better than the best ear can determine and with a stability unattainable by the finest set of tuning forks.


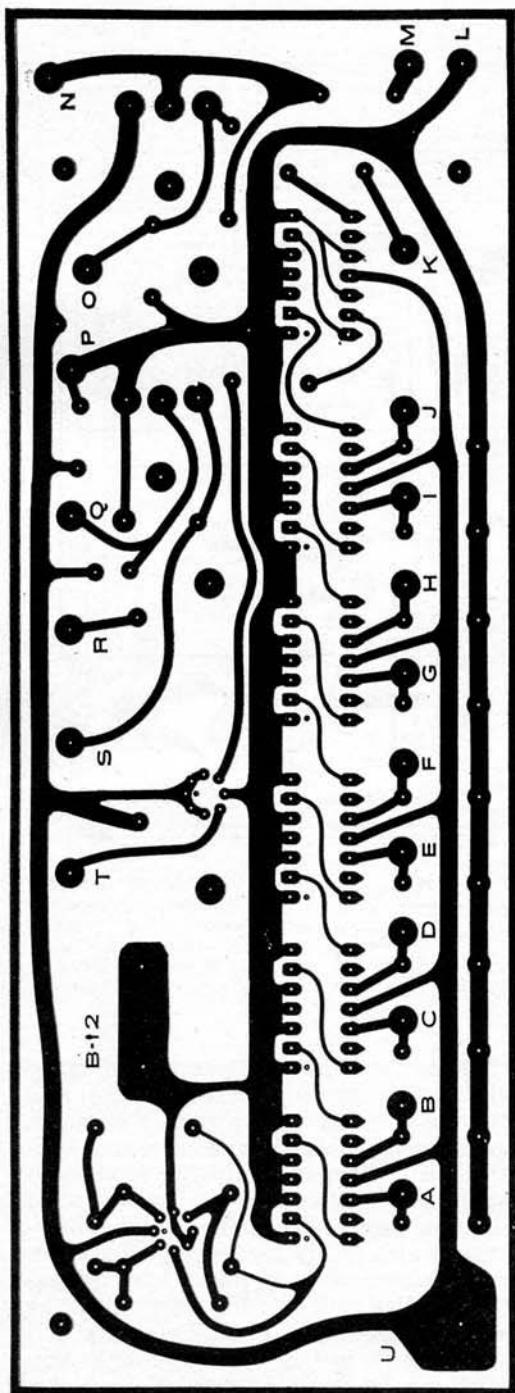


Fig. 2. Actual-size printed-board foil pattern layout. Because of circuit complexity, such a board is necessary to avoid troublesome wiring errors.

contains 8 integrated circuits and two transistors. Depending on the degree of refinement you want, you can build it for \$30 to \$45. Printed circuit boards, dialplates, complete kits, and any special parts are available.

Construction. The schematic of the circuit is shown in Fig. 1. A printed circuit board is mandatory for this project. You can buy one already etched and drilled (see Parts List of Fig. 1) or you can make your own by following the layout guide of Fig. 2. Drilling details are shown in Fig. 3. A clip is riveted to this board to secure the crystal, XTAL. Insert the components as shown in Fig. 4 being very sure that the IC's are positioned and oriented as shown. Units IC1 and IC8 have a flat beside pin 8; the others have a code notch and dot.

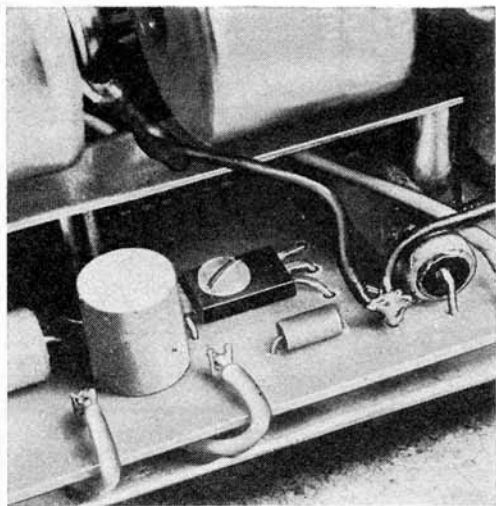The three large holes in the PC board allow you to "double deck" the filter



Transistors are secured to the board metallized-side down, using a plastic screw. Transistors are black, flat rectangles (Q1 shown at center).

capacitors and save some space. Use plastic bolts when mounting Q1 and Q2, and make sure that both are mounted with the metallized side down. A small U-shaped heat radiator should be added to Q2 for extra heatsinking.

The selector switch should be wired in accordance with Fig. 5. Be extra careful with the wiring; any wrong connection will throw off the frequency by at least one note.



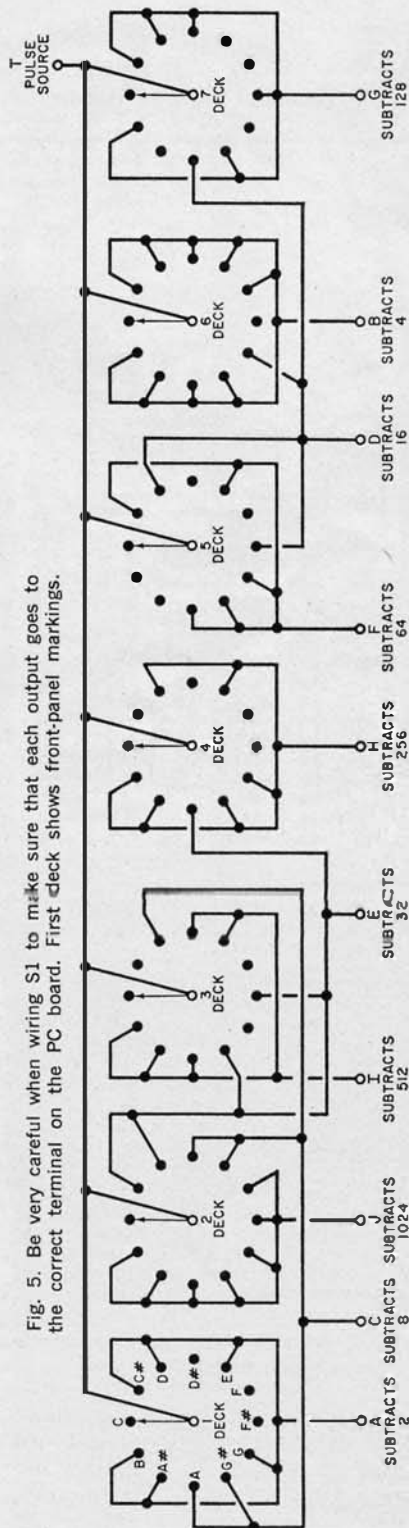


Fig. 5. Be very careful when wiring S1 to make sure that each output goes to the correct terminal on the PC board. First deck shows front-panel markings.

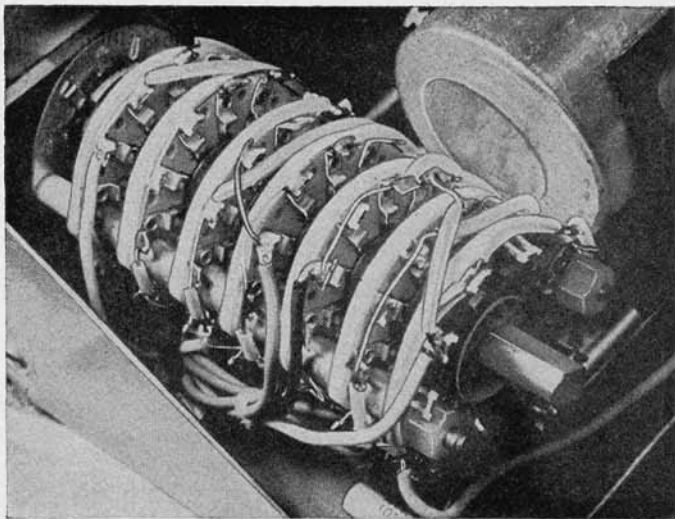


Good wiring practice and neat soldering will ease switch assembly. Use insulated wire where possible.

You can use almost any enclosure you wish, but watch out for any possible mechanical resonance. Fairly large ventilation holes should be provided in the rear to prevent case resonance and any back-pressure effects. The 3×5 oval speaker should be shock-mounted using grommets or some other means. Finally, the grill and grillcloth should be glued in place to prevent any possible rattle from vibration.

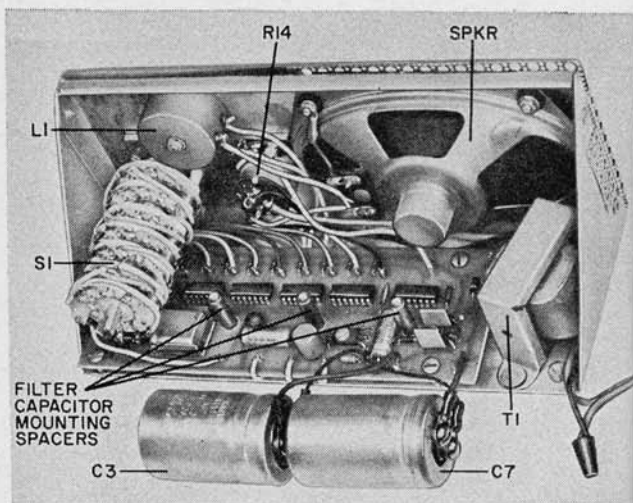


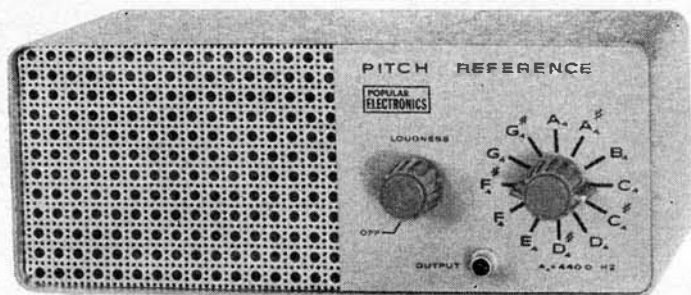Capacitors C3 and C7 "double-deck" over PC board. With a little care, a compact assembly is possible.



The completed Pitch Reference can be dressed up by using a commercially available dial-plate (see Parts List). The cover should have one or two one-inch holes at the rear to prevent any cabinet resonances.

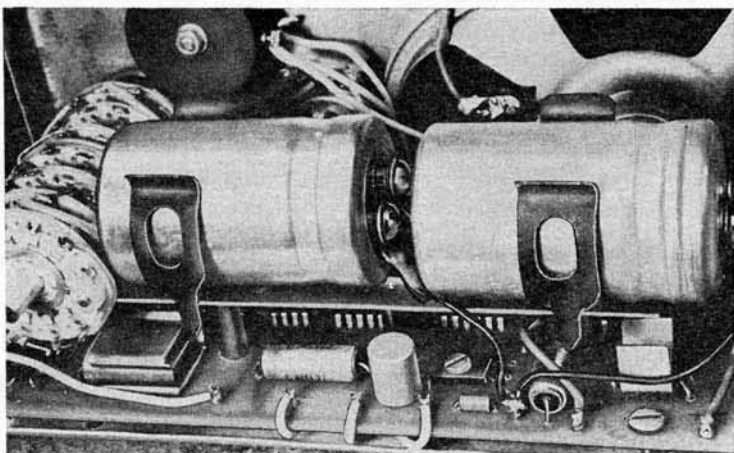The two filter capacitors are clip mounted to a short strip of metal secured to the three spacers. Make sure that the end of the capacitor does not short-circuit any of the switch terminals.



ABOUT PITCH

Each octave of a piano scale consists of 12 notes spread out over a 2:1 frequency range, the frequency of the 13th note being precisely twice that of the first. For centuries, musicians have experimented with absolute pitch and the spacing between individual notes. In common use today, however, is the equally tempered, 12-note scale with A4 (the A above middle C) set at 440.0 Hz.

Equal temperament means simply that there is a constant percentage difference in frequency between every two notes. To get twelve notes equally spaced on a percentage basis over a 2:1 frequency spread, each successive note must be $\sqrt[12]{2}$ or roughly 6% higher or lower in pitch than its neighbor. In this way, slight differences in sharps and flats for the various musical keys are averaged out so that twelve different notes per octave can handle virtually any key.

The 6% interval between notes is called a *semitone*, and musicians call 1/100 of a semitone a *cent*. A 1-cent accuracy in frequency is equal to 0.06%.

Since $\sqrt[12]{2}$ is an irrational number, there is no possible way to generate it exactly, and consequently no way to generate a scale precisely. The question is, "How good can we get?" The very best musicians can sometimes spot a ± 3 -cent cyclic error in pitch, and the very finest tuning forks are only accurate to ± 1 cent. They drift a cent or so for every four degrees F of temperature variation.

The Pitch Reference described here is accurate to ± 0.5 cent, making it twice as good as the best tuning fork you can buy and six times better than the best musician. Being crystal controlled, it is permanently calibrated and does not age or drift over long periods of time.

Operation. Usually, you will set the Pitch Reference to the same note to which you are tuning the instrument. If the instrument is out of tune, you will hear a distinct low-frequency beat note, perhaps several times a second. Adjust

the instrument tuning until the beat note disappears. This is called unison tuning (zero beating). Further adjustment of the instrument will cause detuning in the opposite direction, and a beat note

(Continued on page 103)

CB troublespot. Our "live" monitoring confirmed published reports we have received in the past. There were more than twice as many chit-chatters as legal calls, and violators are still gabbing more than ever without call-signs. The FCC flew in a squad of field personnel several months ago to issue citations and impose monetary forfeitures for such violations.

We monitored with a Messenger 300 portable with battery pack from the eighth floor of our hotel. On channel 4, a feminine voice called "Pacifica" dominated the air talking to "Whistling Turtle!" We also heard tidbits such as, "This is the Bogey man, do you read?" and "Calling Candy Cane!" Would you believe every call was originated by a physically mature adult?

We found that channel 6 in the Los Angeles area was used by intelligently speaking adults, but many of them were bootleggers (individuals who purchase transceivers and put them on the air but have never heard of the FCC or part 95).

Only on channel 9 did we discover CB transmissions conducted in orderly fashion. We learned from Fred Berger, KQY0030, that 9 was generally used by the legal operators in the area. Fred, a monitor for Northeast REACT, shed some light on the conditions in Los Angeles and assured us that all was not as discombobulated as it may have sounded on channels 4 and 6.

San Francisco, Calif. This area seemed as much plagued by skip transmissions as Oklahoma City and L.A., but local conditions were not as deranged as other places. Over a three-day period, transmissions were nearly normal, blemished only by a skip caller from the midwest who wanted to know whether Southern California copied "Indiana Top Dog." He received no answer.

Upcoming: Monitour reports from Philadelphia, Penna., New York City, Hartford, Conn., and Boston, Mass.

I'll CB'ing you,


—Matt, KHC2060

PITCH REFERENCE

(Continued from page 47)

will occur again, the number of beats increasing the farther out of tune the instrument is made. Beat notes may possibly be caused by ear nonlinearity. You'll get the best results if the sound from both the instrument and the reference go in the same ear.

The Pitch Reference can be used to tune octaves other than the one starting at middle C. For example, any C in the scale can be tuned by using the C4 reference. If sufficient volume is not available, an amplifier and speaker system can be connected to the front-panel output jack.

Variations in pitch can be purposely introduced by changing the crystal in the reference to one that is higher or lower in frequency (sharper or flatter in pitch). This is sometimes desirable in tuning certain older instruments and for tuning the extreme octaves on a piano. —

PITCH REFERENCE OUTPUT DATA

NOTE	DIVISION RATIO	APPROXIMATE FREQUENCY (Hz)	STANDARD TRUE FREQUENCY (Hz)
C4	4096	261.6	261.6
C4#	3866	277.2	277.2
D4	3650	293.6	293.7
D4#	3444	311.2	311.1
E4	3250	329.7	329.6
F4	3068	349.3	349.2
F4#	2896	370.0	370.0
G4	2734	392.0	392.0
G4#	2580	415.4	415.3
A4	2436	439.9	440.0
A4#	2298	466.3	466.2
B4	2170	493.8	493.9



Perfect For
POLICE • FIRE
Other Law Agencies • Tow Trucks
• Civil Defense •

Complete with AC and DC power cables, Mounting bracket, less crystals. Crystals \$5.00 ea.

FR-104
(25-50 MHz)
FR-105
(150-175 MHz)

\$140⁰⁰

LISTEN TO: POLICE & FIRE REPORTS

FOR INDUSTRIAL, COMMERCIAL, UTILITY AND GOVERNMENT USE

CRYSTAL CONTROLLED • DUAL CONVERSION • LOW POWER DRAIN

Specifically designed for simplicity of operation and efficiently engineered for dependable service. Fits the smallest autos yet powerful enough to deliver a clean clear signal. Features: 6 crystal controlled frequencies, Dual Limiter, Quadruple tuned RF stage for greater image rejection, Noise Free squelch, PLUG IN crystals for instant freq. change. Compatible with all major continuous tone systems. Operates on 117VAC & 12VDC. Size: 6 1/2" x 2 1/2" x 8 1/2" / Wt: 3 lbs. 8 oz.

SONAR RADIO CORP., 73 Wortman Ave., Bklyn, N. Y. 11207

Please send information on FR-104/105 FM Monitor Receivers. Dept. 701

Name _____

Address _____

City _____ State _____

CIRCLE NO. 28 ON READER SERVICE PAGE