

PART I

PE

# Build the TVT-6: A Low-Cost DIRECT VIDEO DISPLAY

\$35 microcomputer "add-on" provides:

- User-selectable line lengths
- Scrolling
- Up to 4k on-screen characters with only 3-MHz bandwidth

**BY DON LANCASTER** 



Fig. 1. TVT-6 block diagram and truth table for the PROM.

The TVT-6

connected to a KIM-1.

Thanks to some software tricks, a simple and low-cost add-on circuit, and a new way to speed up a microprocessor, you can now build a video interface for your microcomputer for an investment of only \$20 to \$35. The TVT-6 video system described here permits the choice of virtually any format including 16/32 (16 lines of 32 characters), 16/64, or 32/64. It also features full editing capability and full-performance cursor.

In spite of its simplicity (10 low-cost IC's), the circuit employs a new approach to video processing that permits up to 4000 characters to be displayed on-screen within a 3-MHz bandwidth. Although the TVT-6 was designed for the 6502 microprocessor based KIM-1, software can be used to easily map into the JOLT, EBKA, or Ohio Scientific microcomputers. In addition, the TVT-6 can be adapted to other microprocessors, including the popular 6800, 8080, and Z80. It is easiest to use with 16-address-line systems that operate on a single 5-volt supply and 1- $\mu$ s cycle time.



Other systems will require software and microprogramming translation for their particular machine languages.

In this first of a two-part article, we will cover the hardware and construction details for the TVT-6. Next month, we will cover debugging, some useful software for the system, and provide instructions on how to couple the TVT-6 to other microprocessors.

**Circuit Operation**. A block diagram of the TVT-6, as used with the KIM-1 system, is shown in Fig. 1. The complete schematic diagram of the video system is shown in Figs. 2 through 4.

As shown in Fig. 1, bits  $\phi$  through 6 from the "upstream tap" on the KIM display memory drive character generator *IC7* whose blanking and formatting are helped along by the AND gates in *IC6*. The cursor bit (bit 7) is stripped off the upstream tap and routed to cursor blinker *IC5*, which introduces a blinking cursor into the character generator's enable input.

The parallel outputs from IC7 go to



Fig. 3. New SCAN instruction uses PROM IC1, which also has the line length option in its circuit.



Fig. 4. Video combiner (IC10), offset generator (Q1) and sync delay circuits deliver video to TV. Gated clock (IC4) controls parallel-to-serial converter.

C1, C7---0.01-µF Mylar capacitor C2-120-pF polystyrene capacitor C3, C11, C12, C13---0.1-µF Mylar capacitor C4-150-pF polystyrene capacitor C5-2200-pF polystyrene or Mylar capacitor C6-33-pF polystyrene capacitor C8--0.047-µF Mylar capacitor C9-330-pF polystyrene capacitor C10---240-pF polystyrene capacitor D1 through D5-IN4148 silicon diode IC1-IM5610 32×8 PROM (or similar) IC2-74LS00 quad tri-state NAND gate IC IC3---4013 dual-D flip-flop IC IC4-74LS04 hex inverter IC IC5---4011 quad NAND gate IC IC6-74LS08 quad AND gate IC IC7-2513 character generator (must be single-supply type, such as General Instruments No. RO-3-2513)

# **PARTS LIST**

- IC8-74165 PISO shift register IC9-74LS32 quad OR gate IC IC 10-4066 quad analog switch IC J1. J2-Pc-mount phono jack (Molex No. 15-24-2181 or similar) Q1-2N4402 or MPS6523 (Motorola) transistor The following resistors are 1/4 watt, 10% toler-R1, R10---470 ohms
- ance
- R2-10,000 ohms
- R3.R7-220 ohms
- R4,R16,R17,R18-2200 ohms
- R5.R6--22.000 ohms
- R8,R13,R19---4700 ohms
- R9-2.2 megohms

The serial video from IC8 goes to the TV Bandwidth Compensator in IC9, which predistorts the video by delaying the video output and OR'ing it against itself. This widens the vertical portions of all characters to generate clean and crisp characters that require minimum bandwidth. The amount of widening is determined by C2 (Fig. 4). The optimum value of C2 is obtained when the generated M or W in the video display just barely closes.

R11-100 ohms

- R12-1000 ohms
- R14,R15-100,000-ohm pc-type (upright) potentiometer
- Misc .- Sockets for IC's (seven 14-pin, two 16-pin, one 24-pin); 36-contact edge connector with 0.156" centers (Amphenol 225 or similar); solid hook-up wire for jumpers; insulated sleeving; test-point terminals (5); solder; etc.
- Note: The following items are available from PAIA Electronics, Box 14359, Oklahoma City. OK 73114: No. PVI-1PC printed circuit board for \$5.95; complete kit of all parts, No. PVI-1K, for \$34.95 (specify blank or KIM-1 programmed IC1); KIM-1 coded cassette, with programs, No. PVI-ICC, for \$5.00. All prices postpaid.

shift register IC8, where they are converted into a serial video signal. The clock and load commands for IC8 come from gated oscillator IC4, which derives its signals from the microcomputer's clock. It is important that the correct clock phase be selected to permit the loading of IC8 to occur when the output of the character generator is valid and settled. This is phase 2 in the KIM-1. (If you are using a different µP based computer, check this detail.)

The vertical and horizontal timing signals from IC2 in the gating circuit are delayed by IC3. The display positioning can be varied by potentiometers R14 and R15. The vertical and horizontal sync signals are combined with the enhanced video from IC9 into video combiner IC10. The output from IC10, available at J1, is composite video, with the sync tips at ground, black at 0.4 volt, and white at 1.6 volts. This output can be used to drive conventional video monitors and converted TV receivers. The video output from *IC10* is also fed to Q1, which is offset to deliver a +4-volt output for the white level. This output, available at J2, can be connected directly to the first video amplifier of most transformer-powered solid-state TV receivers (see box for details) without requiring biasing, coupling, or translation circuits.

Two options are provided with the TVT-6, both of which are jumper selected. The LENGTH option allows a choice of either 32 or 64 characters/line. The CURSOR option gives the choice of either no cursor or allows the cursor to be displayed under software control.

**Construction.** The actual-size etching and drilling guide for the printed circuit board used in the TVT-6 is shown in Fig. 5, along with the component-installation diagram. Start assembly by installing and soldering into place the 21 jumpers and test points. (Note that insulated sleeving must be used on two of the long jumpers.) Install the IC sockets, resistors, capacitors, diodes, jacks, and position controls *R14* and *R15*. Do not install the IC's at this time. The correct IC installation sequence and the waveforms to be observed will be discussed in Part 2 next month.

**Computer Interface**. Detailed in Table I are the requirements of each of the edge connector contacts on the TVT-6 and how to use each contact. Table I also contains the KIM-1 interface connection instructions. The interface consists of adding a new connector and making some add-on connections. One circuit board trace is cut on the KIM-1's pc board to permit an optional changeover switch (or jumper) to be added to the microcomputers. This permits KIM-1 to be used with or without the TVT-6.

**General Operation**. Since most of today's TVT circuits are used with a microprocessor or microcomputer, it is best to do as much of the display control as possible with the microprocessor and some software. What may not be obvious is that almost all of the timing in the system can also be done using the microprocessor. All this takes is a few dozen words of code.

The four key secrets of operation for the TVT-6 are:

1. Carefully choose how the address lines are defined for TVT operation.

2. Add a new instruction, which we call SCAN, to rapidly address 32 or 64 sequential memory locations.

3. Permanently connect an upstream





Fig. 5. Actual-size foil pattern (top) and component installation (below). Use sockets for all IC's. Edge connectors go to KIM-1.

50

# TABLE I TVT-6 PINOUT AND KIM-1 INTERFACE

TVT-6							
CONTACT	NAME	REMARKS					
1,2	GND	Heavy wire to expansion contact 22 or simi-					
3 4 5	NC	Snares					
5, 4, 5	VCI	Spares					
0	VOL	(In other systems cl					
		locted so that load of	ulso arrivos when CG is				
		valid.)	uise arrives when CG is				
7,8,9,10,	VD7,	Data output from n	nemory display; drives				
11,12,13,	VD6,	character generator.	. For KIM-1 to display				
14	VD5,	any part of pages 0	0 through 03, connec-				
	VD4,	tions must be mad	le as follows:				
	VD3,	TVT-6 contact:	to pin 12 of KIM-1 IC:				
	VD2,	7	U5				
	VD1,	8	U6				
	VDΦ	9	U7				
		10	U8				
		11	U9				
		12	U10				
		13	U11				
		14	012				
15	CSI	Display memory chip	select from µP; nega-				
		tive logic OH combin	red with IVI-6 chip se-				
10	000	Disalay managed	FON KIM-1.				
16	CSU	Display memory chip select source; enables					
		display memory whe					
		through 112 in KIM	. Goes to pin 13 of US				
		nart of pages 00 th	-1 when displaying any				
		connection in KIM 1	must be broken				
17		Decode enable: doe	s low when up is oper-				
• • •	DLIN	ated in normal mod	le high when TVT-6 is				
		doing an active sea	n Goos to KIM 1 Ap				
		nlications contact K	Any external ground on				
		applications contact I	K should be removed				
18 19 20	Δ11	Address inputs from					
21 22 23	A12	dresses Ard A6 th	rough A10 not sent to				
24 25 26	A13	TVT-6. Connections	to KIM-1 expansion:				
27, 23, 20,	A14	KIM-1 contact:	to TVT-6 contact				
21	A15.	N (A11)	18				
	A5.	P (A12)	19				
	,						

	A4,	R (A13)	20		
	A3,	S (A14)	21		
	A2,	T (A15)	22		
	A1	F (A5)	23		
		E (A4)	24		
		D (A3)	25		
		C (A2)	26		
		B (A1)	27		
28, 29, 30,	DB7,	μP data bus; tri-state	e active high from IC1		
31,32,33,	DB6,	during active scan, n	ot used at other times.		
34, 35	DB5,	Connections to KIM-1	expansion:		
	DB4,	KIM-1 contact:	to TVT-6 contact:		
	DB3,	8 (BD7)	28		
	DB2,	9 (DB6)	29		
	DB1,	10 (DB5)	30		
	DBφ	11 (BD4)	31		
		12 (DB3)	32		
		13 DB2)	33		
		14 (DB1)	34		
		15 (DBΦ)	35		
36	+5V	Regulated +5-volt ( should be heavy wir sion contact 21 or sin in TVT-6.	egulated +5-volt (200-mA) power bus; nould be heavy wire. From KIM-1 expan- on contact 21 or similar point to contact 36 TVT-6.		

Note: KIM-1 conversion consists of breaking one foil trace and adding a new 36-pin socket (Amphenol 127 or similar). Connection to be broken originates as K $\phi$ (pin 1 of U4). Routing of K $\phi$ that goes to memory chip select pin 13 of U5 through U12 should be broken. Other K $\phi$  connections, such as that to pin 1 of U16 should remain intact. Any external ground connections to Application connector contact K (decode-enable) must be removed. All wiring should be made with a wiring pencil.

When KIM-1 is used *without* displaying video, it will behave normally and transparently as long as TVT-6 is plugged in and addresses 8000 through DFFF are not used. To restore KIM-1 operation with TVT-6 out of socket, or to use available addresses for other programs, jumper pin 15 to pin 16 and separately jumper pin 1 to pin 17 in the KIM-1. Note that this jumpering is to be done only when TVT-6 is out of its connector. I you wish, a dpdt changeover switch can be added to perform the jumpering. Switch positions should be changed only when power is off.

memory tap to the character generator and display circuit.

4. Create special software that will allow TVT-6 scanning.

All 16 address lines are used, assigned as shown in Fig. 6A for a 32-character/line system or as shown in Fig. 6B for a 64-character/line system. Address A15 is the horizontal sync pulse and the key to jumping to the new SCAN instruction. This pulse is followed in descending address order by the vertical sync (A14) and three lines (L4, L2, L1) that produce the "what row of dots do we want?" information for the character generator. The lower address lines are used to select a page of display memory and to select the character that goes into any particular horizontal and vertical location on the display.





# **DIRECT-VIDEO INPUT CONVERSION**



Adding a TVT-6 direct-video input to a small-screen solid-state TV receiver requires only two short lengths of shielded coaxial cable, as illustrated in the schematic. (Important Note: *Do not use a holchassis TV receiver!* Make absolutely certain that the TV receiver you use is transformer powered from the ac line.) The conversion circuit shown here is for the Sears No. 562-50260500 (Sams Photofact No. 1565-1). Other TV receivers can be modified in a similar manner.

The data within the machine (see Fig. 6C) uses the lowest seven bits as ASCII character storage. This is arranged by putting the least-significant ASCII character bit in the least-significant data slot, and so on up through the more significant bits. The eighth data bit (DB7) is reserved for a cursor. If DB7 is a zero, a character is displayed, while if it is a one, a cursor box is optionally displayed.

The existing KIM-1 keypad can be used as an ASCII keyboard for many applications, particularly for setup and debugging. If you wish to add an external ASCII keyboard and encoder, connect it to the KIM-1's parallel interface A, following the assignments shown in Fig. 6D. The seven ASCII bits go to the seven low-order data lines, while PA7 is hard wired for a zero. The keypress, or strobe, signal from the keyboard must pull the IRQ (interrupt request line) to ground for 10  $\mu$ s to enter a character or machine command.

The truth table for PROM IC1 is shown in Fig. 1. This truth table stores the SCAN instruction, activated by addresses 8000 through DFFF. When IC1 is enabled, it causes the microprccessor's program counter to appear on the address lines for 32 or 64 consecutive scans that advance one count per microsecond. This automatically and sequentially addresses the display memory and produces exactly the data needed for a horizontal scan of TVT characters. The scan instruction runs at least twice as fast as the microprocessor normally moves, which is the key to TVT timing with a microprocessor.

er performance to video access. Correct bias is provided by TV output of the TVT-6. As an option, you can defeat the sound trap in the Sears TV receiver by lifting one end of capacitor *C201*.

The earphone jack in the circuit provides

automatic changeover from normal receiv-

To use the SCAN instruction, jump to a subroutine whose starting address is within the 8000 to DFFF range. For example, if you call JRS 8200, the SCAN instruction will deliver a horizontal sync pulse and initiate operation on the top row of characters, starting with the first character on page 2. After a selected 32

interrupt and reset vectors on the KIM-1 so that the operating system will work compatibly and properly with the new SCAN instruction,

There are many possible codings for the SCAN program with the limitation that the last address is a return-to-subroutine (RTS) instruction. The obvious choice of NOP or EA runs at only half speed and can't be used. Of the three dozen instructions that operate at full speed, the choice of LDY is the one that does not disturb the accumulator or its flags. This adds flexibility to other programs. The Y register can be viewed as a write-only memory in the SCAN software and we can think of the whole SCAN instruction as a group of double-speed fetch-butdon't-execute instructions. Theoretically, a 64-word PROM would be required for a 64-character line, but this can be overcome by ignoring address  $A\phi$  and changing the PROM's address every second cycle of the machine.

**Upstream Tap**. The SCAN instruction will sequentially address 32 or 64 memory slots per horizontal scan line at a rate of one-per-clock cycle (1  $\mu$ s). These addresses are presented to the entire memory in the computer, including the memory to be displayed. However, during the display times, the SCAN instruc-



or 64 characters, the SCAN instruction automatically jumps back to the main program.

The scan instruction can be viewed as a "portable subroutine" because it readily moves around to automatically output the correct page and character generator's row information, starting with an easily computed JSR address. Addresses above DFFF will not activate the scan instruction. This includes the tion and its PROM have control of the data bus so that the display memory (or anything else) cannot output information to the data bus.

The upstream tap is added as shown in Fig. 7. This tap is always outputting information to the character generator in the TVT-6. The output information is present even (and especially) when the display memory data bus drivers have been inactive.  $\diamondsuit$ 



AST MONTH, we discussed construction of the TVT-6 TV typewriter and explained how it works and how it is connected to a KIM-1 microcomputer. We also started a discussion of the operating secrets of the TVT-6. Here, we complete the "secrets" discussion and go on to system debugging, some useful programs, and tell you how to interface the TVT-6 with other microprocessors.

**Software.** Four examples of tested, annotated, and workable KIM-1 software are given in the tables in this article. Table II contains a  $16 \times 32$  scan program with full interlace. It automati-

# BUILD THE TVT-6 Part II

System debugging, software, and how to interface to other processors.

# BY DON LANCASTER

cally generates almost all the timing required by the TVT-6 and its companion TV monitor for this display format. The program is run by jumping to memory location 17Ad. The display is stopped by interrupting with the operating system, the cursor, or other program.

Table III is an optional full-performance cursor for the  $16 \times 32$  system and includes scrolling, full cursor motion, and erase-to-end-of-screen capabilities. It is run by allowing the keypress signal from the keyboard to interrupt the scan program (any of the three Tables) via the IRQ interrupt line. Note that the cursor program is totally independent of the SCAN program. The only things the two programs share in common are the same pages of display memory. The screen-read-to-cassette can be performed using the existing KIM-1 operating system programs. You can also load from cassette to display, using the automatic search firmware.

Table IV is a 16-line/64-character scan program that requires only 64 words to be written into memory for the entire program. This program can be used to display the entire 1k of minimum KIM-1 memory for use as a super frontpanel display if desired. For display-only applications, 1k of contiguous memory



#### TABLE II

### 16 line X 32 character per line Interlaced TVT6 Raster Scan:

	ц S	µP - 6502 System - KIM-1		Sta End	rt - JMP 17Ad - Interrupt	Displayed 0200-03PP Program Space 1780-17E2		
	HS	VS	[4]	12 1	L1 0	1 V8 V4	4 V2 V1 H16 H8 H4 H2 H1	
			Uppe	er Add	lress		Lower Address	
	1780 1781 1784 1785	NOP STA PHA PLA	EA 8d 48 68	(8A)	(17)	Equalize 2 of Store upper Equalize 10 Continued	cycles address cycles	
	1786 1788 178b 178b	BNE JSR ADC CMP	d0 20 69 C9	00 00 08 C0	80	Continued ////Characte Increment Ch Is VS = 1?	er Scans 1-8//// heracter Scan Counter	
		BCC JSR JSR TAX	90 20 20 AA	FO* (EO) 00	(17) 80	No, do next Equalize 15 ////Characte Save Upper /	character scan cycles via sub er Scan 9//// Address	
	1798 179b 179d 179d	LDA ADC STA TXA	Ad 69 8d 8A	(89) 1F (89)	(17) (17)	Get Lower Ad Increment L; Restore lowe Get Lower Wo	ddress ; Set C on V4 overflow er word; save carry ord	
	17A1 17A3 17A4 17A6	BNE NOP ADC JSR	d0 EA 69 20	00 CO 00	80	Equalize 5 c continued Add carry; F ////Characte	cycles Reset VS er Scan 10////	
T	17A9 17Ab 17Ad 17Ad 17b0	CMP BCC LDA EOR	C9 90 Ad 49	84 d3* (dP) 80	(17)	Is it line ' No, continue Get Interlac Change field	*17"? e character scans ce word 1	
	17b2 17b4 17b7 17b9	BMI STA LDX JSR	30 8d A2 20	05* (dF) 66 (EO)	(57) (17)	Jump if ever Odd Field V Load short r Equalize 15	n field Sync; Restore Interlace word number of VB scans cycles via sub	
	17bC 17bF 17C1 17C1 17C4	JSR BPL STA LDX	20 10 8d A2	(EO) 05* (dP) 67	(17) (57)	Equalize 15 Jump if odd Even Field W Load long nu	cycles via sub again field V Sync; restore interlace umber of V Blank scans	
	17C6 17C9 17CA 17Cb	JSR CLD PHA PLA	20 d8 48 68	1E	80	////1st V bl Equalize 9 c Continued Continued	lanking scan //// cycles	
	17CC 17CE 17d1 17d3	LDA STA LDA STA	A 9 8d A 9 8d	00 (89) 82 (8A)	(17) (17)	Initialize 1 Continued Initialize u Continued	lower address	
	17d6 17d9 17dA	JSR CLC DEX	20 18 CA	00	80	///Remaining Initialize c One less sca	g V Blanking scans//// carry an	
-	17db 17dd 17dd 17dP 17E0	BMI BPL BCS	30 10 80 60	A4* Ed*		Start Charac Repeat Verti Interlace wo ///Equalize	cter scan Lcal blanking scan ord storage 15 SUBROUTINE ////	
	17E2	RTS	60			Continued.		

NOTES: TVT6 must be connected and scan microprogram PROM (IC1) must be in circuit for program to run.

Both 17b4 and 17C1 require that page 17 be enabled when page 57 is addressed. This is done automatically with KIM-1 circuitry.

Step 1788 goes to where the upper address stored in 178A and the lower address stored in 1789 tells it to. Values in these slots continuously change throughout the program.

For a 525-line system, use 17b8 64 and 17C5 65 and a KIM-1 crystal of 992.250 kHz. This is only needed for video superposition and titling applications.

Normal program horizontal frequency 15,873.015 Hz; Vertical frequency 60.0114 Hz. 63 us per line; 264.5 lines.

\* Denotes a relative branch that is program length sensitive.

( ) Denotes an absolute address that is program location sensitive.

TVT6 length jumper must be in "32" position.



is required. Keep in mind that the KIM-1 has some operating system slots in the top of page zero and the stack at the top of page one. Unless you actually want to display the stack and operating system parameters, do not use these slots.

The 64-character line makes the TV receiver's horizontal frequency run considerably lower than normal. This will require a readjustment of the horizontalhold control or some extra capacitance across the existing horizontal-hold capacitor. The width of the raster may also have to be reduced; this is most easily accomplished by adding a low-value inductor in series with the yoke. These changes are best made in a smallscreen, transformer-powered monochrome TV receiver. The tradeoff of a lowered horizontal frequency produces a long character line but still allows 1 µs/character. This will not tax the bandwidth restrictions of TV receivers or r-f modulators. (Editor's Note: The smallscreen Sears TV receiver we used required adjustment of horizontal size and linearity, a 0.033-µF Mylar capacitor in parallel with the 0.068-µF capacitor used for C408 in the receiver, and an inductor consisting of 60 turns of No. 24 enameled wire on a 1/2" Nylon form in series with the red yoke lead in the receiver. In addition, it was necessary to disconnect one side of C201 in the receiver

#### **POPULAR ELECTRONICS**

-STAR



to defeat the sound trap. Never attempt to modify a TV receiver that is powered directly from the ac line without an isolating transformer.)

Table V contains a program that we call "Cruncher the Bear." This program produces 64 fully interlaced characters in each of 32 rows, for a total of 2048 sharp ASCII characters on-screen at one time within the 3-MHz bandwidth. You can add a hex-to-ASCII converter that slowly sequences high- and low-order machine code characters in the same slot and end up with 4096 hex characters displayed in only 3 MHz of bandwidth.

Table V requires a contiguous 2k of memory with a common upstream tap and separate chip enables. However, it is easily incorporated if you really want or need to display as many characters as the program allows.

Other software is easily written and developed for the TVT-6. For example, you may wish to have a  $32 \times 44$  or a  $32 \times 48$  character display and still use normal, or nearly normal, horizontal scanning rates. This allows for video titling and superimposition, oversize characters, color graphics, lower-case characters, and game displays. There is no lower limit to the number of character rows or characters per line you can use. If you have limited memory available, AUGUST 1977



(Continued on next page.)

#### Table III (Continued)

	018E	JSR SEC	20 (Cb)	(01)	Clear last line Set Carry				
	0192 0194	BCS LDA	b0 P0* A5 (Ed)		Restore Cursor to start of last line ////Cursor Up/////Get Cursor				
	0196 0197 0199	SEC SBC STA	38 E9 20 85 (Ed)		Set Carry Move up one line Restore Cursor				
0144	-0196	BCS	b0 Ad*		Underflow of page?				
	019F 01A1	LDA	A9 01 C5 (EE)		Did screen underflow?				
0144	-01A3	BNE	d0 A5*		No, Pinish Yes, Home Cursor				
	01A7 01A9 01Ab	DEC LDA CMP	C6 (Ed) A9 FF C5 (Ed)		///Cursor Left////Decrement Cursor Set A to page underflow Test for page underflow				
019d	-01Ad -01Af	BEQ	FO EE* do 99*		Change Page if off Page Pinish if on page				
	0161	PHA	48		Save Upper cursor location				
	01b4 01b6 01b7	LDA PHA	A5 (Sd) 48 20 (Cb)	(01)	Get lower cursor location Save lower cursor location				
	OIDA	PLA	68	(01)	Get lower cursor location				
	O1bb O1bd	STA PLA	85 (Ed) 68 85 (FF)		Restore lower cursor Get upper cursor location				
0144	-0100	BNE	d0 88*		Pinish				
	0102	LDA STA	A9 00 85 (Ed)		///SUB//Home Cursor/// Set lower cursor to zero				
	01C6 01C8	LDA STA	A9 02 85 (EE)		Put page 2 in A Set upper cursor to 0200				
r*	01CA 01Cb	RTS LDA	60 A9 20		Return to main program ///SUB//Enter Space///				
L	01Cd 01d0	JSR BNE	20 (d3) d0 F9*	(01)	Enter space via Sub Repeat if not to end				
	01d2 01d3	RTS STA	60 91 (Ed) E6 (Ed)		Return to main program ////SUB//Spter,Increment// store				
	0107	BNE	d0 06*		Overflow?				
Γ	01d9 01db	INC LDA CMP	E6 (EE) A9 04 C5 (EE)		Yes, Increment cursor page to 03 Load A with page 4 Teat for Overflow				
4	-Oldf	RTS	60		Return to main program				
	NOTES: IRQ vector must be stored in 17FE 00 and 17FF 01.								
Total available stack length is 32 words. Approximately 16 are used by operating system, cursor, and scan program. Stack must be initialized to OIFF as is done in KIM-1 operating system. For 30 additional stack locations, relocate subroutings attriting at OIP2 algorithms									
	To protect page, load OOP3 04. To enable entry load OOP3 0								
Cursor address is stored at $OOEd$ low and $OOEE$ high on page zero.									
To display cursor load 014d 80. To not display cursor load 014d 00.									
	* Denotes a relative branch that is program length								

sensitive.

( ) Denotes an absolute address that is program location nsitive.

you can run  $8 \times 32$ ,  $4 \times 64$ ,  $1 \times 64$ , or even 1 × 8 character formats. All this takes is software changes, and the circuitry of the TVT-6 remains the same.

Initial Debugging. At this point, there should be no IC's in the sockets of the TVT-6 board assembly. Start by connecting the LENGTH jumper to 32 and the CURSOR jumper to YES on the TVT-6 board. (Note: These points are pads located at the center of the circuit board, not the edge-connector contacts.) Temporarily insert a jumper wire between pins 3 and 14 on the IC5 socket. Center the two position control potentiometers and install IC1, IC2, and IC6 in their respective sockets.

Connect your video monitor to the TVT-6 board and power up the system. Check for the presence of the SCAN instructions (see PROM Truth Table in Fig. 1 of Part 1) at hex locations 8000 through 8020. Write a simple program that jumps to a subroutine at location 8000 and then loops. Single-step through this program to verify proper operation of the SCAN instruction. Do not



# **USING THE TVT-6 WITH OTHER POPULAR MICROPROCESSORS**

Both parts of this article have used the TVT-6 with the 6502 microprocessorbased KIM-1 microcomputer. Here is how to use the TVT-6 in LC's that use other popular microprocessors.

6800. The 6800 µP is very similar to the 6502 and, therefore, is easiest to convert. The SCAN microprogram can be LDAB(C6) for words 0 through 30 and RTS(39) for word 31. A literal translation of the tightest part of the SCAN program (1D;1782 through 178C) is: JSR(BD); ADDA(8B); STA(B7); CMPA(81): BCC(24). This routine requires 25 µs to cycle through as compared to the 21 µs required for the 6502.



8080. A stock 8080 µP can normally change its program counter once every 2 µs, but it can be "tricked" into doubling its speed during a SCAN microprogram by driving the usual address line A9 of the display memory from SYNC. The SCAN microprogram is then NOP(00) for words 0 through 30 and RET(A9) for word 31. A tighter than literal translation of the SCAN program (1D;1782 through 178C) is: STAXB(02); CALL(AD); ADD(82); CMP(BB); JNC(DB), which requires 24 µs to cycle through. Here, the TVT-6 address lines A5 through A1 must be relabelled A4 through AØ, respectively.

**280.** The Z80  $\mu$ P can use 8080developed software with speed-doubling scans, or it can simply be run faster, allowing the program counter to change once every microsecond. Use a literal translation of the program for the 6502.

12 Address Line  $\mu$ P's. The four upper address lines of 12 address line  $\mu$ P's can be decoded to allow normal operation, 8 to 12 lines of scan, a vertical sync pulse, an operating return system, and an optional "page-change" command. This leaves a 256-character page on the bottom eight bits, and the "page-change" command can be latched to change to any number of additional pages, as required.

**General Hints.** Horizontal scan should last at least 62, 63.5, or 64 µs for conventional ho izontal-frequency operation. The microprogram scan must *end* exactly this number of microseconds later for each horizontal line in the total scan program. The total number of lines must produce a vertical frequency between 59.9 and 60.1 Hz per field. Note that a portion of the RTS time will be spent during the active (microprogram) scan time. Horizontal scans that last longer than 85  $\mu$ s may make it difficult to obtain TV interface.

You can shorten a *blank* microprogram active scan by an *even* number simply by jumping ahead when you call your subroutine. For example, a JSR 8000 may produce a 32-character scan, while a JSR 8002 can produce a 30-character scan. This approach can come in handy when there is a need for equalizing scan lengths between character rows and during vertical retrace.

	TABLE IV						
	16 line X 64 character per line TVT6					VIO R	<u>(aster Scan</u> :
		µ₽– Syste	6502 m - KIM-	1 En	art - JMP 17AA 1 - Interrupt		Displayed 0000 - 03FF Program Space 1780-17bE
	ĦS	VS	14 12	L1 0	V8 V4 V2	<u>V1</u>	H32 H16 H8 H4 H2 H1
		Up	per Addr	ess			Lower Address
Γ	1780 1782 1785 1785 1788	LDA STA JSR ADC	A9 80 8d (87) 20 00 69 08	) (17) 80	Initialize Up Store Upper / ////Character Increment cha	pper Addre r Sca aract	Address 285 ans 1-8//// ter scan counter
	178A 178C 178E 178F	CMP BCC TAX LDA	C9 C0 90 F4* AA Ad (86)	(17)	Is VS = 1? No, Do next o Save Upper Ad Get lower add	chara ddres dress	acter scan 38 3
	1792 1794 1797 1799	BCS JSR BCS ADC	b0 00 20 04 b0 00 69 3F	80	Equalize 3 cy ////Character Equalize 3 cy Increment Low	ycles r Sca ycles wer;	s an 9//// s Set C on V2 overflow
	179b 179E 179F 17A2	STA TXA JSR ADC	8d (86) 8A 20 00 69 C0	) (17) 80	Restore Lower Get upper add ////Character Add Carry; Re	r Add drees r Sca eset	dress; save carry an 10//// VS
- START	17A4 17A6 17A8 17A8	CMP BCC BCS CLD	C9 84 90 dA* b0 00 d8		It is "Line 1 No, continue Yes, Go to ve Equalize 2 cy	17"? char ertic ycles	racter scans cal blanking scans
	17AD 17AE 17D0 17D2	JSR LDX LDA STA	20 00 A2 22 A9 00 8d (86)	CO (17)	////Vertical Load #V Blank Initialize Lo Continued	Sync k Sca ower	e Scan//// ans -2 Address
1	17b5 17b6 17b8 17b8	CLC BCS JSR DEX	18 b0 00 20 00 CA	80	Equalize 2 cy Equalize 2 cy ////Vertical One less scar	ycles ycles Blan	s again king Scans////
L	17bC	BMI BPL	30 C2* 10 P5*		Start Charact Repeat Vertic	ter S cal H	Scan Blanking scans
	NOTES	5: T	VT6 must ust be i	t be con In circu	nected and sca it for program	an mi m to	icroprogram PROM (IC1) run
Step 1785 goes to where the upper address stored in 1787 and the lower address stored in 1786 tells it to. Values in these slots continuously change throughout the program.							
Normal program horizontal frequency is 11,764.705 Hz. Vertical Prequency is 60,024 Hz. 85 us per line; 196 lines. Character time 1 us. 160 active lines, 36 retrace. Needs TV set adjustment and possible modificat (hold and width).							cy is 11,764.705 Hz. 85 us per line; 160 active lines, ent and possible modificatio
		•	Denotes	a rela lve.	tive branch th	hat i	is program length
		( 9	) Denot ensitive	tes an a	bsolute addres	ss th	nat is program location
		т	VT6 len	th inmr	er must he in	"6A	" position

proceed beyond this point until you are certain that the SCAN subroutine is operating properly. (Critical waveforms to be observed with an oscilloscope are illustrated in Fig. 7 using the program listed in Table II.)

Insert *IC3* into its socket and load the program given in Table II. (*Never* install an IC in a powered circuit; always turn off the power, install the IC, and power up again.) Set the address to 17Ad and depress GO. Using an oscilloscope, check at test point VR for the presence of a 60-Hz pulse. Switch the scope to line-sync and observe that the pulse remains fixed or drifts very slowly across the screen. Again, do not proceed until you are certain that the SCAN program is operating properly. Install all remaining IC's, except *IC5*, in their respective sockets on the TVT-6 board. At this point, the screen should be filled with a stable display of 512 cursor boxes. Viewed up close, the boxes should appear to be "hiding" characters. Do not proceed until you have the indicated display.

Checking with Fig. 7, particularly with respect to the LOAD and CLOCK on *IC8* (Fig. 7A) verify whether or not the appropriate waveforms are present. If they are, remove the jumper wire from the *IC5* socket and install *IC5*. Now, the screen of the monitor should have displayed on it a full array of characters with about half of them winking cursor blocks. Load the following hex numbers into memory, starting at location 0200:





20, 20, 20, 50, 4F, 50, 55, 4C, 41, 52, 20, 20, 45, 4C, 45, 43, 54, 52, 4F, 4E, 49, 43, 53, 20, 20, 54, 56, 54, 2D, 36, 20, 20. Return to address 17Ad and depress GO. The top display line should now read "POPULAR ELECTRONICS TVT-6" and be indented three spaces. If all is well to this point, you can begin feeding in your cursor programs, add external keyboard and/or cassette loads and dumps, etc.

Should you encounter problems with your TVT-6, always begin debugging by using the  $16 \times 32$  format on a KIM-1, even if you plan on using longer line lengths or plan to translate the code into another coding system. Note that the translation *must* be at the machine-language level because the SCAN program must provide the exact number of machine cycles as well as the proper sequencing. The 64-character lines will require some adjustments to be made in the monitor TV receiver's horizontal circuit as detailed earlier.

**Closing Remarks.** We have presented here full construction and operating details for a very versatile and inexpensive TV typewriter for use with the KIM-1 microcomputer. If you have a computer that uses a microprocessor other than the 6502 used in the KIM-1, we refer you to the box for use details.



TABLE V CRUNCHER THE HEAR Program for a 32 line X 64 character per line TVT6 raster scan: µP - 6502 Start - JMP 17CO Displayed 0000-07FF System - KIM-1 End - Interrupt Program Space 1780-17dA HS VS L4 L2 L1 V16 V8 V4 V2 V1 H32 H16 H8 H4 H2 H1 Upper Address Lower Address Initialize Upper Address Store Upper Address ////Character Scans 0-7//// Increment Character Gen by 2 LDA STA A9 8d 1780 80 (87) (17) 1782 1785 JSR 20 00 80 1788 ADC 69 10 178A CMP BCC C9 90 CO F4\* No, Do next character scan Save Upper Address Get Lower address 178E PHA 48 (86) (17) 178F T.DA Ad Increment L; Set Carry on V2 overflow Restore L; Save carry Get Upper Word ///Character Scans 8,9 //// ADC STA PLA 1792 69 1794 8d 68 (86) (17) 1798 JSR 20 oc 80 Add Carry; Reset Upper Address Is it "Line 33"? No, repeat Character Scans Get Interlace word 1790 ADC 69 CO CMP BCC C9 90 179d 88 E11 LDA Ad (81) (17)17A1 Set Carry if Odd Pield finished Start Even Pield if Carry Clear Load Even number of V Scans -2 Load Even Pield Upper Start ADC BCC 69 90 78 0C\* 1744 1746 17A8 17AA LDX LDA A2 22 A9 80 Even Fielá V Sync + Restore Interlace Even Field Line 33 CMP Value Store Even 33 CMP Value Clear Accumulator 17AC (81) STA 84 (57) 88 (95) LDA 17AF A9 8d 17h1 STA (17) 1764 00 A9 LDA 1766 STA 84 (86) (17)Initialize Lower Address Equalize 31 cycles continued 17b9 - 17bb - 17bC LDY A0 88 06 DEY Pd BPL 10 continued 17bE BCS **b**0 OC\* Jump if even field Load Odd Pield Upper Start Odd Field V Sync + Restore Interlace Odd Pield line 33 CMP Value -START T.DA 1700 A9 88 STA 1702 8d (81) (57) 1705 LDA AG 90 8d A2 20 17C7 17CA STA LDX (9E) (17) Store Odd 33 CMP Value Load Odd number of V Scans //// 1st V Blanking Scan //// Equalize 7 17CC 17Cf JSR 3P 80 PHA 48 1740 PI.A 68 continued 1741 CLD d8 Equalize 4 17d2 17d3 continued //// Other V Blanking Scans //// CIC JSR 20 00 80 DEX 1746 CA One Less scan Start Character Scans BMI 30 1707 A7\* +1749 BPT. 10 F6\* Repeat V Blanking Scan NOTES : TVT6 must be connected and scan microprogram PROM IC1 must be in circuit for program to run. TVT6 length must be in circuit for program to run. jumper must be in "64" position. Step 1785 goes to where the upper address stored in 1787 and the lower address stored in 1789 tells it to. Value Values in these slots continuously change throughout the program. Step 1781 is 80 for even fields and 88 for odd fields. Step 179E is 88 for even fields and 90 for odd fields. Both 17AC and 17C2 require that page 17 be enabled when page 57 is addressed. This is done automatically with page 57 is addre RIM-1 circuitry. Note that 2K worth of contiguous memory from 0000 to 07PF is needed. This takes a KIM-1 modification. Both sets of 1k words must share a common upstream tap but be separately enabled. Normal program horizontal frequency is 11,764.705 Hz. Vertical Frequency is 59.8712 Hz. For 60 Hz vertical use 1.002150 MHz crystal. 85 us per line; 196.5 interlaced lines per field; two fields per frame. One us character time, 160 active lines per field. Needs TV set adjustment and possible modification (hold and width). \* Denotes a relative branch that is program length sensitive.

( ) Denotes an absolute address that is program location sensitive.